
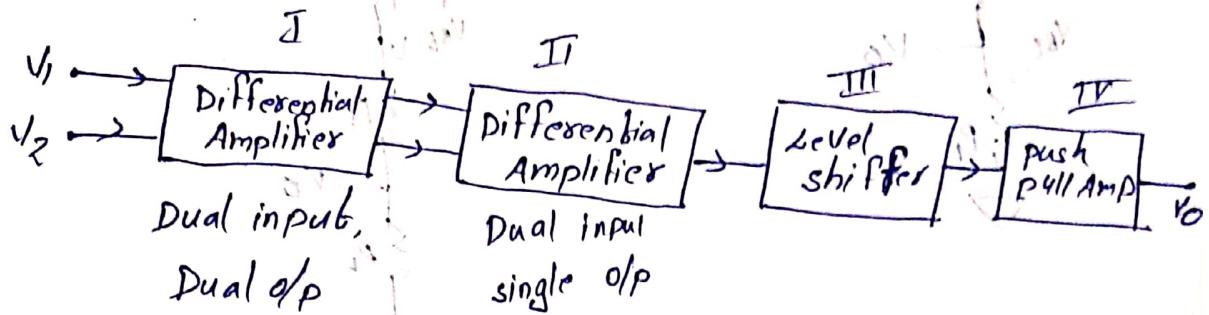


operation Amplifier

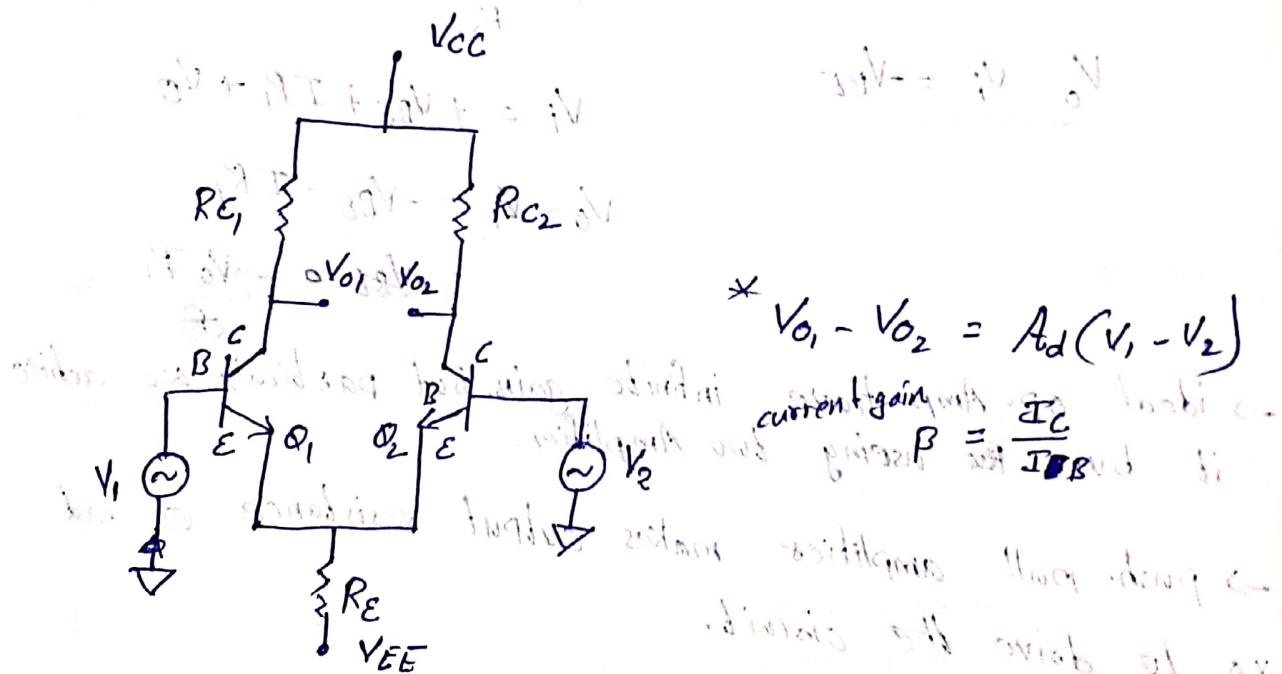
op-Amps is a high voltage gain amplifiers.
op-Amps basically have 4 blocks




Differential Amplifier



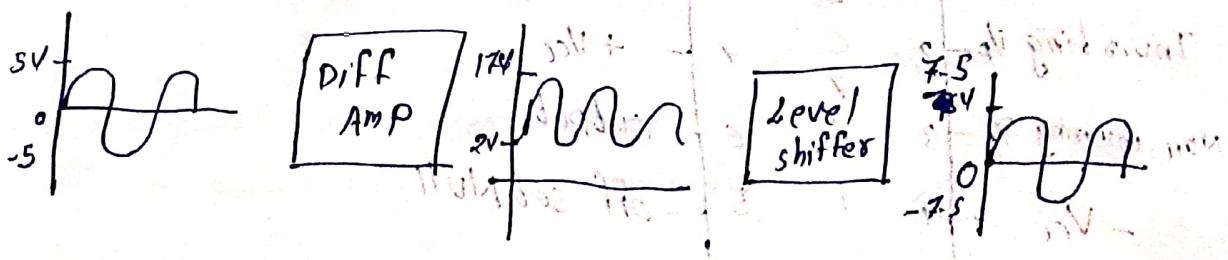- Maximum gain in an opamp achievable in diff. Amp.
- Both have same current gain.
- In II stage we take outputs as V_{01} , Ground.
- R_C coupled Amplifiers $\Rightarrow R_C$ allows only mid range frequencies



level shifter :-

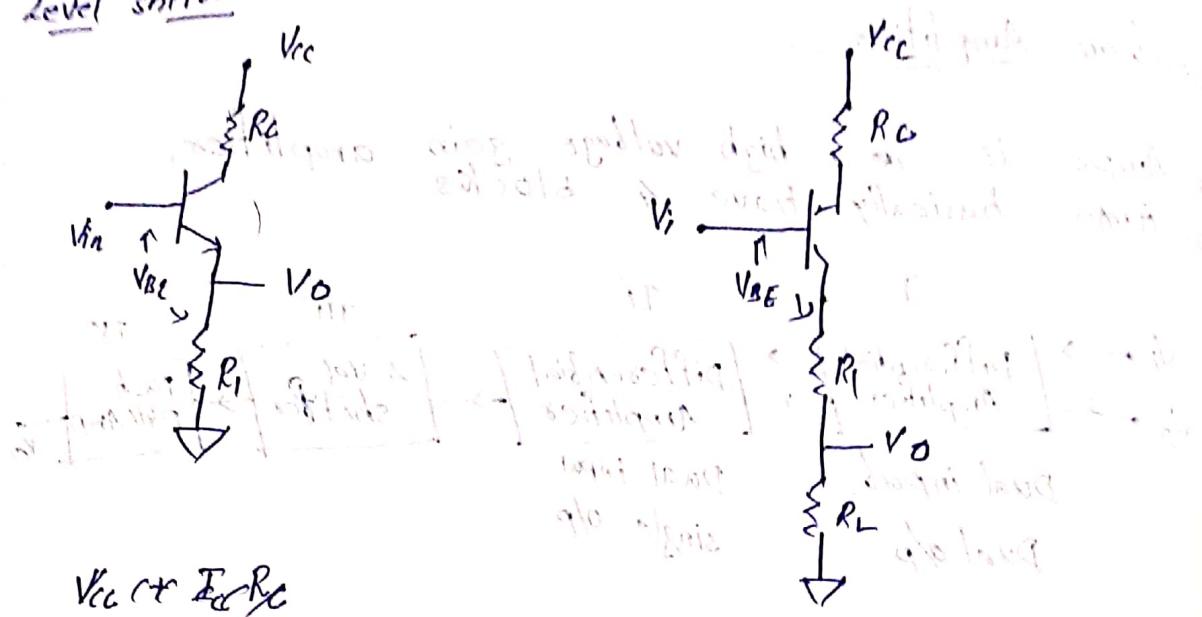

$$V_{cc} + I_c R_c$$

$$V_C = V_i \approx I_c R_C$$

$$\underline{V_o - V_i = -V_{BE}}$$

$$I_E = \frac{V_o}{R_2}$$


$$V_i = +V_{BE} + I R_1 + V_o$$

$$\underline{V_o = V_i = -V_{BE} - I R_1}$$


$(V_o - V_i)_{\text{dc}} = 0V - 0V$
 → ideal op-amps have infinite gain. But practically we achieve it by using two amplifiers.

→ push-pull amplifier makes output resistance O_o and to drive the circuit.

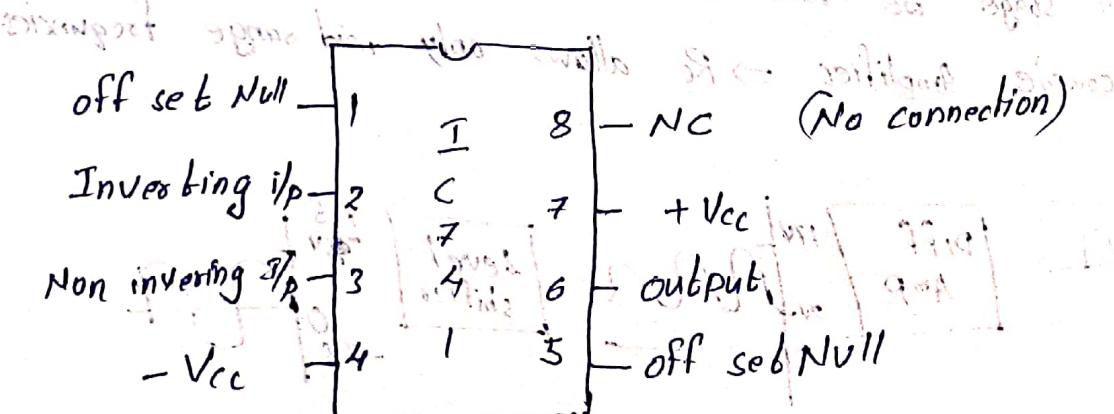IC 741 - opamp has three terminals: inverting input, non-inverting input, and output.



symbol :-

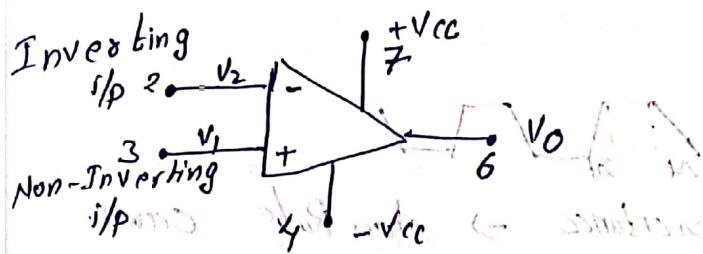

Note with end of Non Invert. and Invert.

Ideal Practical

Gain (A_0)

∞

10^6

i/p Resistance

∞

$10M\Omega$ to $100M\Omega$

o/p Resistance

$0 - \infty$

$5k\Omega$ to $10^6 \Omega$

CMRR

∞

10^6 or $120dB$

Band width

∞

$120dB$ (a) $90dB$

slope Rate

∞

$0.01 V/\mu s$
 0.5 to $1 V/\mu s$

To make the current zero, input resistance is made infinity so that Transistors won't break and the Power consumed by Amplifier is minimum.

→ O/p Resistance is low. Because the output voltage should not drop across resistance so we can provide maximum voltage output.

→ CMRR - Common Mode Rejection Ratio = $\frac{Av}{Ac}$ → differential mode
Notice → Ac → common mode.

→ Band width is maximum to allow more channels (more frequencies) in the Amplifier.

→ Rate of change of o/p voltage w.r.t time.

$$\text{slow Rate} = \frac{dV_o}{dt}$$

i/p



- due to unavoidable parasitic capacitance \Rightarrow slow Rate occurs.
- ideally there should not be any time delay.
- so, slow Rate is infinity.

$$V_o = A_d(V_1 - V_2)$$

$$\text{If } V_1 = 0$$

$$V_o = A_d V_2$$

$$\text{If } V_2 = 0$$


$$V_o = A_d V_1$$

V_1, V_2 are out of phase Due to Diff. Amp

above condition

Ideal characters:

Voltage Transfer characteristics:

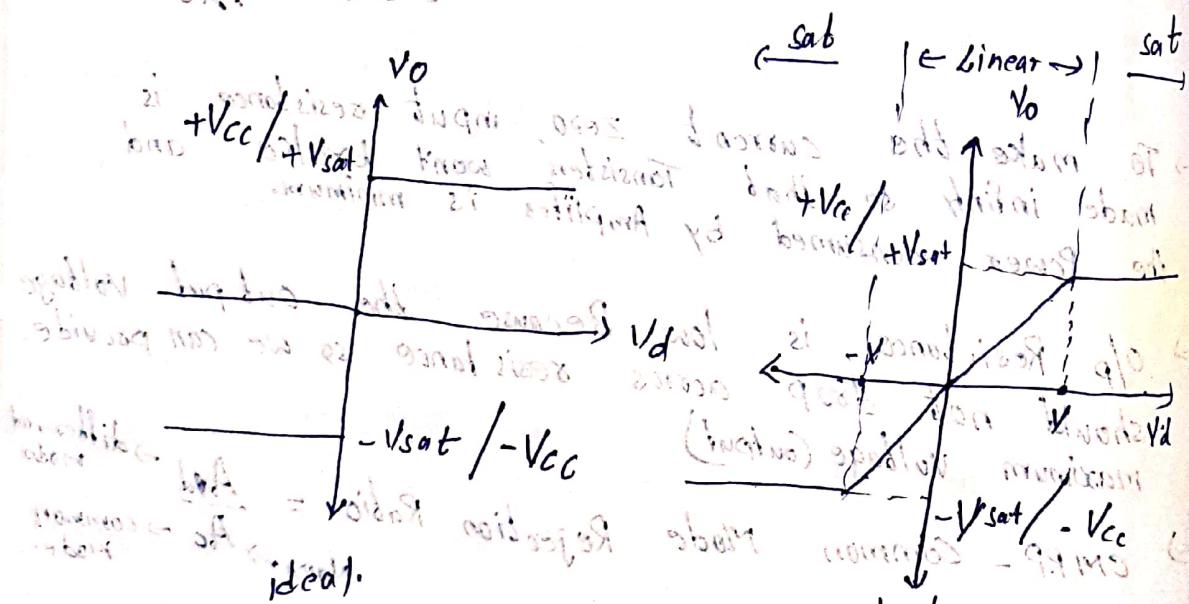

standard model with no limitation

$$V_o = V_i - V_{sat} \text{ and } V_i = \frac{V_{sat}}{A}$$


practical.

small load resistor \Rightarrow no limitation

V_{out} = A V_d

$V_o = A(V_d - A(V_1 - V_2))$ to signals to other voltages
 Two Regions Linear Region → Amplifiers
 saturation Region → comparators/switch

Input Bias Current (I_B) nA

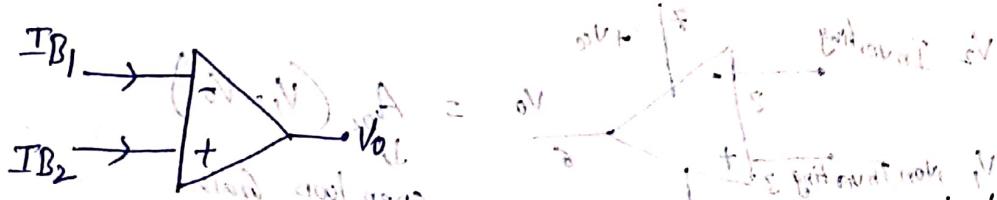

The average current entering into the inverting + non-inverting terminal.

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


The input offset current (I_{io}): nA
 The difference of inverting and non-inverting bias current.

$$I_{io} = |I_{B1} - I_{B2}|$$

input offset voltage (V_{io}): 1mV or 1MV

It is the difference of input voltage applied to the op-amp in order to nullify the output.

$$V_{io} = V_1 - V_2$$

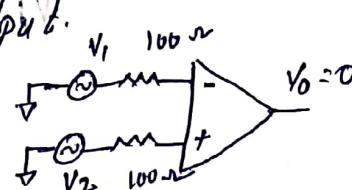

output offset voltage (V_{oo}): mV
 If I_B is a non-zero output voltage when both the input voltages are zero.

Thermal Drift:


The rate of change of voltage with respect to change in temperature is called Thermal Drift.

$$\frac{\Delta V_o}{\Delta T} \text{ mV/C} \leftarrow \text{higher with higher } \frac{\Delta V_o}{\Delta T}$$


V_{IO} , I_B , I_{BQ} - changes due to Temperature.

$$\text{mV/C } \mu\text{A/C } \mu\text{A/C}$$

A_{OL} (AT) changes with Temperature

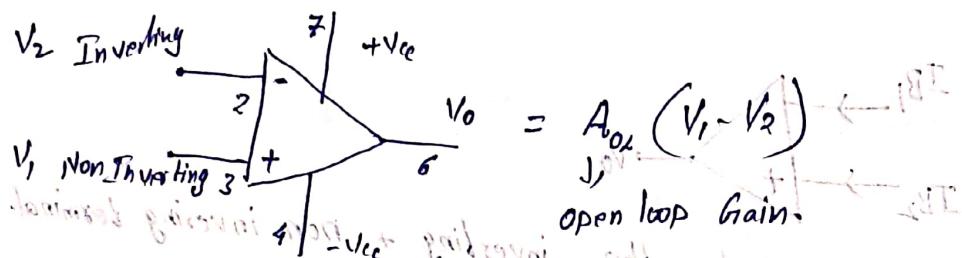

Inverting Amplifier:

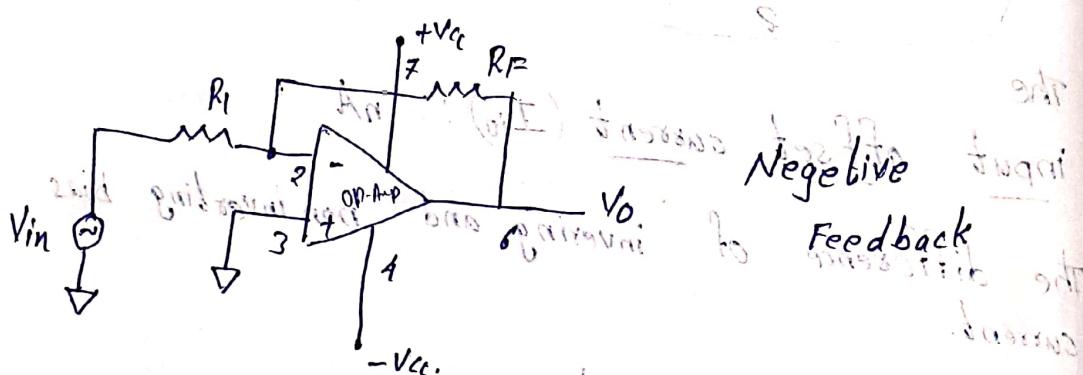

$$\text{Gain } (A) = \frac{V_o}{V_{in}} = -\frac{R_F}{R_1} = \frac{(AT - \text{AT}_0)}{S} = \text{AT}$$

$$V_{dd} = V_{1+} - V_{2+} = 0$$

Virtual Ground.

Now anti-symmetry $R_1 \rightarrow \infty \Rightarrow I_{B1} = I_{B2} = 0$

$$V_2 = V_2$$

$$\frac{V_2 - V_{in}}{R_1} + \frac{V_2 - V_o}{R_F} = 0$$


$$V_i = V_o = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_o}{R_F} = 0$$

$$V_o = \left(-\frac{R_F}{R_1} \right) V_{in} \Rightarrow \frac{V_o}{-V_{in}} = \frac{R_F}{R_1}$$

$$Gain = \frac{V_o}{V_{in}} = \frac{-R_F}{R_1}$$

Non-Inverting Amplifier

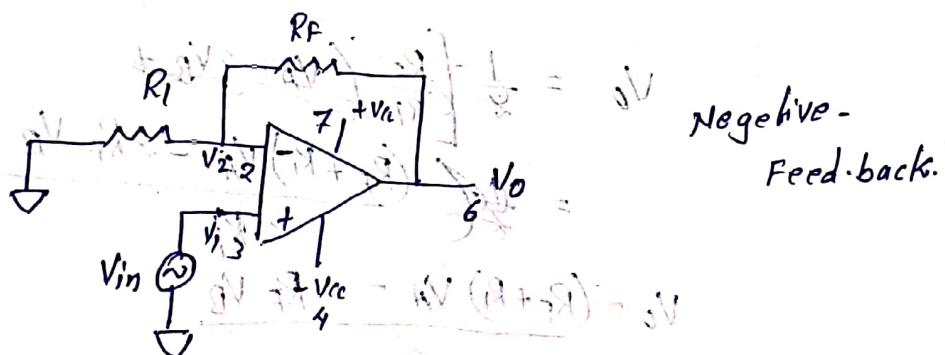

$$A = \frac{V_o}{V_d} = \infty \quad V_d = 0$$

$$V_{in} = V_2$$


$$\frac{V_2}{R_1} + \frac{V_2 - V_o}{R_F} = 0$$

$$\frac{R_F}{R_1} V_{in} = V_o - V_{in}$$

$$V_o = V_{in} \left(\frac{R_F}{R_1} + 1 \right)$$

$$Gain = \frac{V_o}{V_{in}} = \frac{R_F}{R_1} + 1$$

Subtractor Amplifier :-

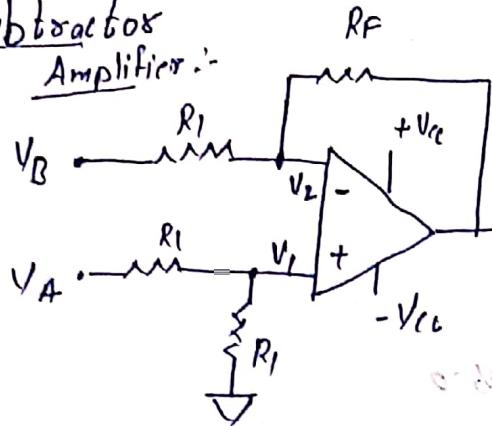

$$\frac{V_1}{R_1} + \frac{V_A - V_A}{R_1} = 0 \quad \text{and} \quad \frac{V_2 - V_B}{R_1} + \frac{V_2 - V_0}{R_F} = 0$$

$$\frac{V_A}{2} = V_1 \quad \text{and} \quad \frac{V_2 - V_B}{R_1} = \frac{V_0 - V_2}{R_F}$$

$$R_F \left(\frac{V_A - V_B}{2} \right) + \frac{V_A}{2} = V_0$$

$$V_0 = \frac{1}{2} \left[R_F \left(\frac{V_A - 2V_B}{2} \right) + \frac{(R_F + R_1)V_A - 2R_F V_B}{2R_1} \right]$$

$$V_0 = \frac{(R_F + R_1)V_A - 2R_F V_B}{2R_1}$$

$$= \frac{1}{2} \left(\frac{R_F + 1}{R_1} V_A - \frac{R_F}{R_1} V_B \right)$$

$$= N \cdot I_o + V_o$$

$R_1 = R_F \rightarrow$ Subtractor Amplifier


$$V_o = V_A - V_B$$

$$(1 + \frac{R_F}{R_1}) V_o = V_A - V_B$$

$$1 + \frac{R_F}{R_1} = 2 \rightarrow R_F = R_1$$

open loop \rightarrow Compensation
closed loop \rightarrow Negative feedback \rightarrow decrease gain
Amplifier.

Integration :-

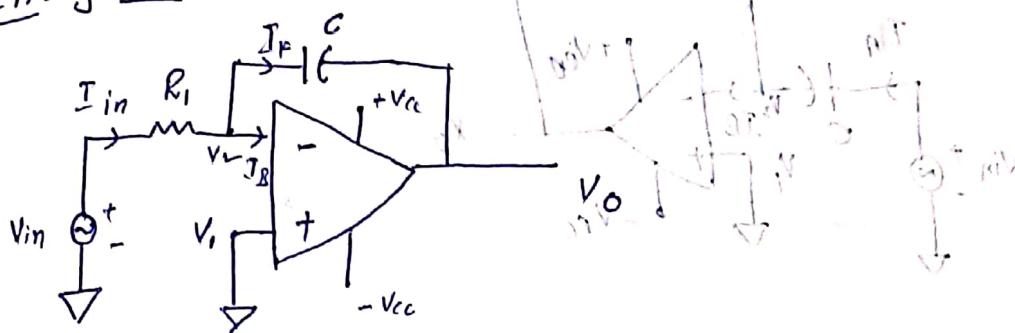

$$V_i = 0 \Rightarrow V_2 = 0 \quad (\text{By virtual ground})$$

$I_B = 0$ for an op-amp

$$\Rightarrow -\frac{V_2 + V_{in}}{R_1} = I_F \quad \frac{dV}{dt} = \frac{dV}{dt}$$

$$I_F = \frac{+V_{in}}{R_1} \quad I_F = C \cdot \frac{dV}{dt}$$

$$C \cdot \frac{dV}{dt} = \frac{+V_{in}}{R_1}$$

$$dV = +V_{in} \frac{dt}{R_1 C}$$

$$V = \frac{1}{CR_1} \int_{t_0}^t V_{in} dt \quad \text{Apply integration w.r.t time.}$$

$$V_2 - V_o = \frac{1}{CR_1} \int_{t_0}^t V_{in} dt$$


$$V_o = -\frac{1}{CR_1} \int_{t_0}^t V_{in} dt$$

$$V_o = \frac{-1}{R_1 C} \int_{0}^t V_{in} dt$$

scaling factors $\rightarrow R_1, C \quad T = R_1 C$

$$V_o \propto \frac{1}{T}$$

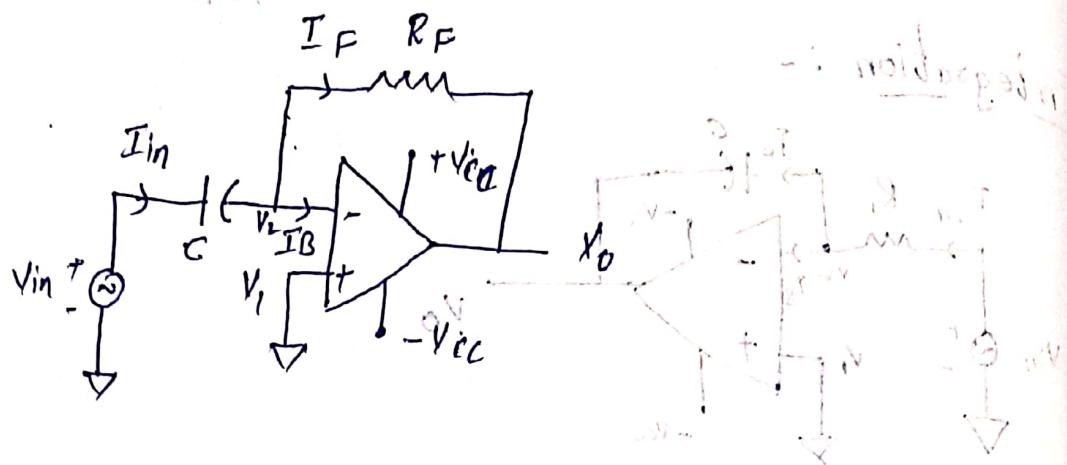Differentiation: conversion of alternating voltage into derivative voltage



By virtual ground $V_1 = 0 \Rightarrow V_2 = 0 \Rightarrow V_0 = 0$


$$I_{in} = I_f$$

$$\frac{V_o}{R_f} = -\frac{V_0}{R_f}$$

$$c \frac{dV_{in}}{dt} = -\frac{V_0}{R_f}$$

$$V_0 = -R_f C \frac{dV_{in}}{dt}$$

Logarithmic differentiation

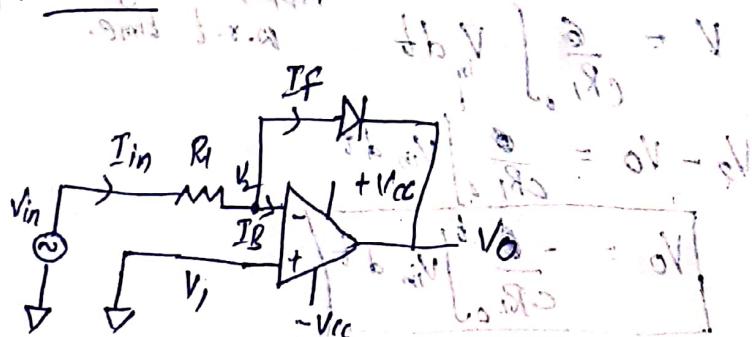

$$\sqrt{\frac{V_0}{V_{in}}} = \frac{1}{R_f} \cdot \frac{dV_{in}}{dt}$$

$\ln \frac{V_0}{V_{in}} = \frac{1}{R_f} \cdot \frac{dV_{in}}{dt}$

$\ln V_0$

diode current:

$$I_d = I_{do} \left(e^{\frac{-V}{V_T}} - 1 \right)$$

I_{do} : Reverse saturation current

V - diode voltage

V_T - Thermal voltage = 26 mV

$$I_{do} \left(e^{\frac{-V}{V_T}} - 1 \right) = \frac{V_{in}}{R_1} \quad \log_{10} = 0.4343 \ln e$$

$$e^{\frac{+V_o}{V_T}} - 1 = \left(\frac{V_{in}}{I_{do} R_1} \right)$$

$$e^{\frac{-V}{V_T}} \gg 1$$

$$\frac{V_o}{V_T} = \log \left(\frac{V_{in}}{I_{do} R_1} + 1 \right)$$

s.t. one is
neglected.

$$V_o = V_T \ln \left(\frac{V_{in}}{I_{do} R_1} + 1 \right)$$


$$\frac{V_{in}}{R_1} = I_{do} e^{\frac{V_o}{V_T}}$$

$$\frac{V_o}{V_T} = \log V_{in} + \log R_1 - \log I_{do}$$

$$V_o = V_T \ln V_{in} - V_T \ln R_1 - V_T \ln I_{do}$$

$$V_o = K \ln V_{in}$$

anti-logarithmic (exponent)

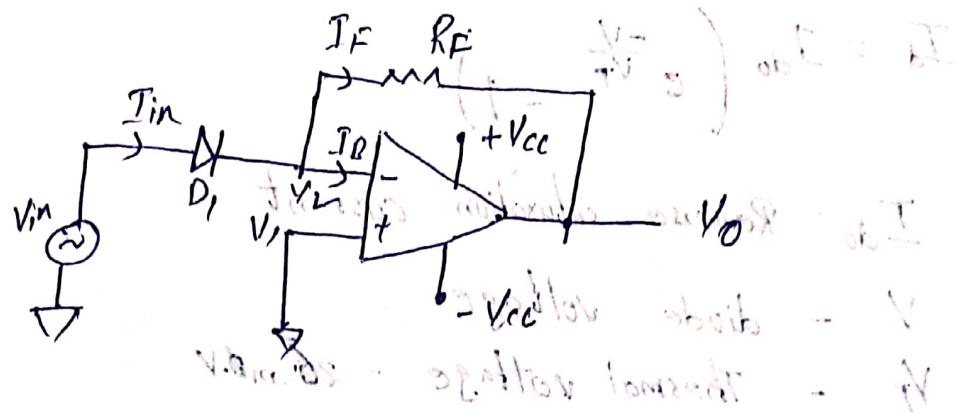

$$I_{in} = -\frac{V_O}{R_F} = (\log(V_{in}/V_t)) \text{ stat.}$$

Annotations: "addition = prod." and "diff = 1/e"

$$I_{do} \left(e^{-\frac{V_{in}}{V_t}} - 1 \right) = +\frac{V_O}{R_F}$$

$$e^{-\frac{V_{in}}{V_t}} \approx 1 - \frac{V_{in}}{V_t}$$

$$\Rightarrow \left(1 + \frac{I_{do} R_F}{V_t} \right) \approx -\frac{V_O}{V_t}$$


$$-\frac{V_O}{V_t} \approx +V_t C^{-V_{in}}$$

$$V_t = \frac{V_{cc}}{R_F}$$

$$V_t = \frac{V_{cc}}{R_F}$$


$$V_t = \frac{V_{cc}}{R_F}$$

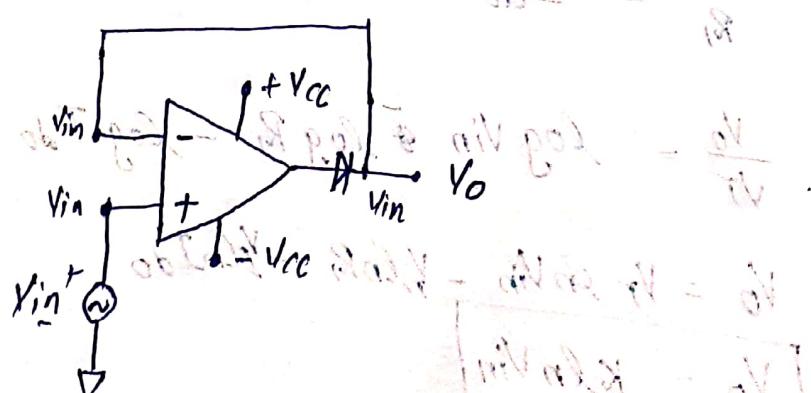Precision Rectifier :- super diode - idle diode



$$V_o =$$


ideal diode

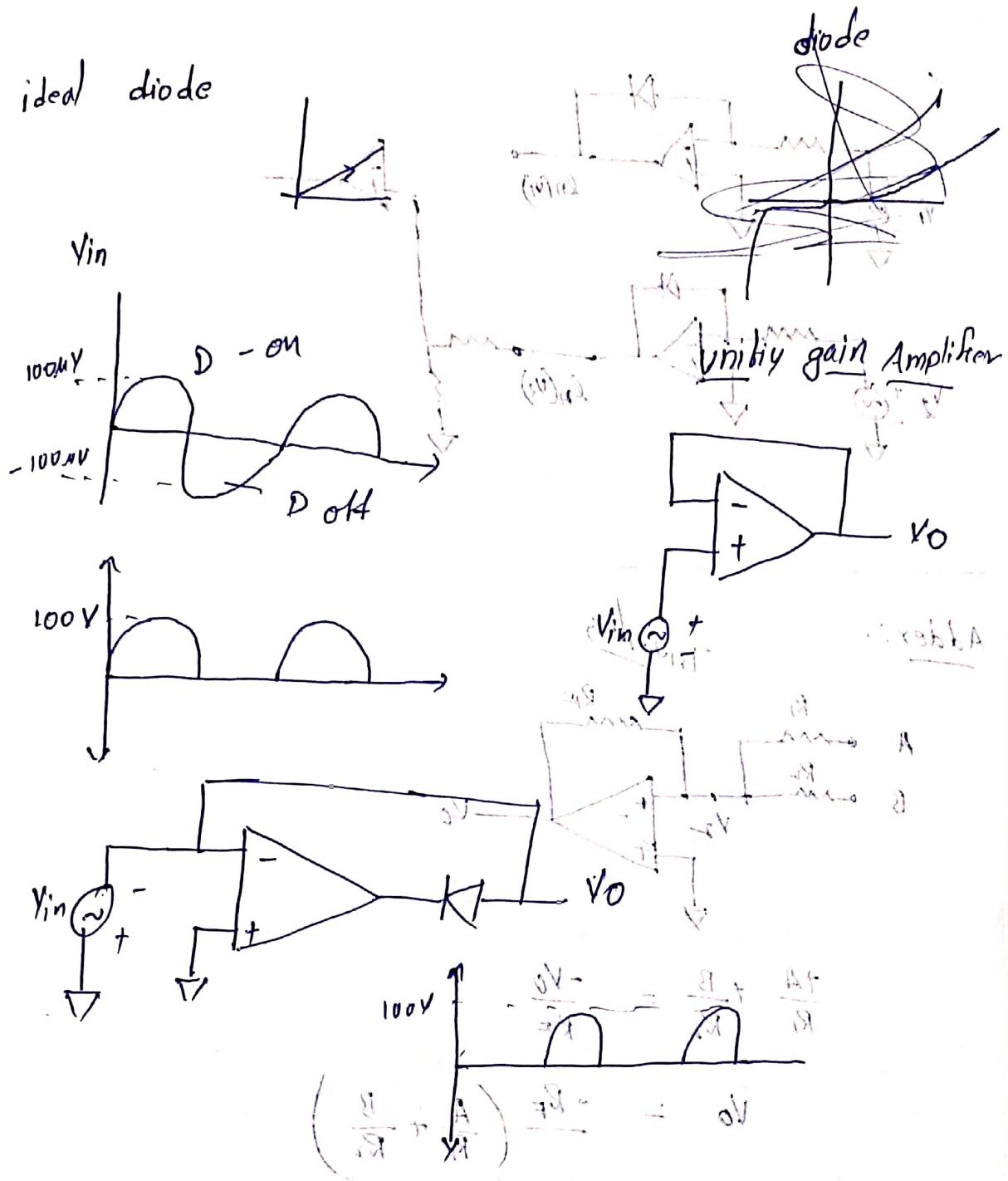


Multiplication :-


$m \times n$ ✓
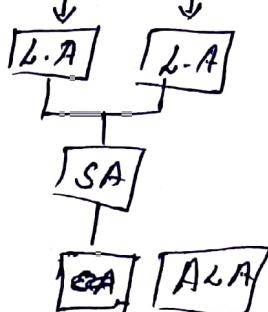
$$\text{for } \ln(m \times n) = (\ln m^2 + \ln n)$$



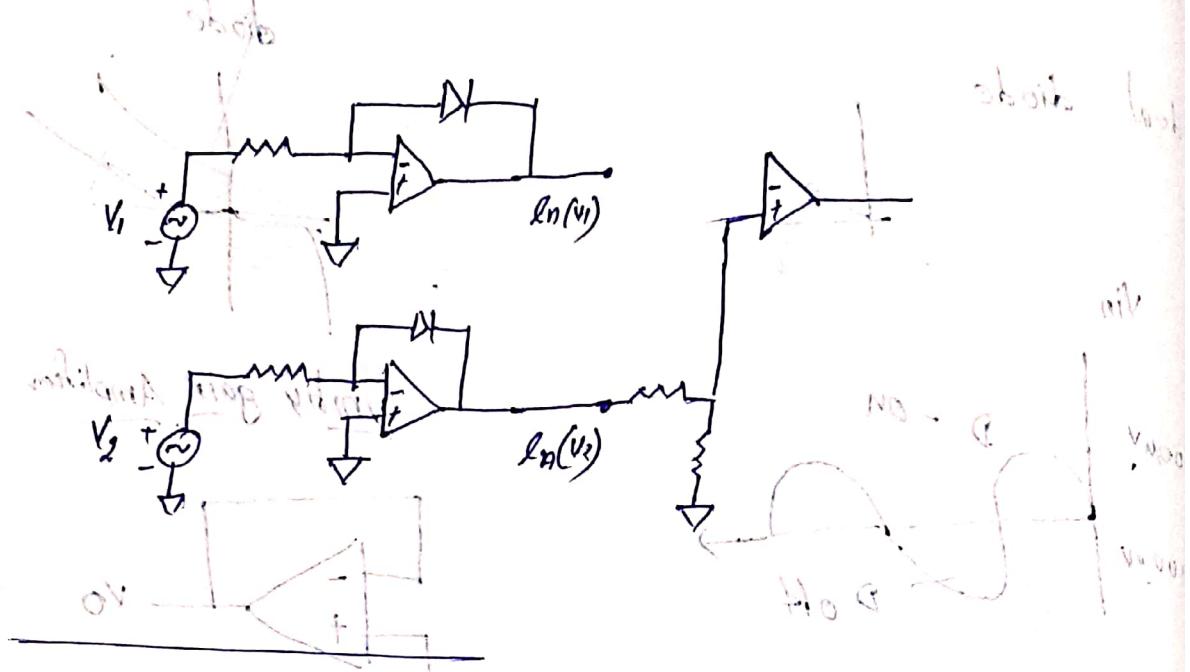

Adder :-

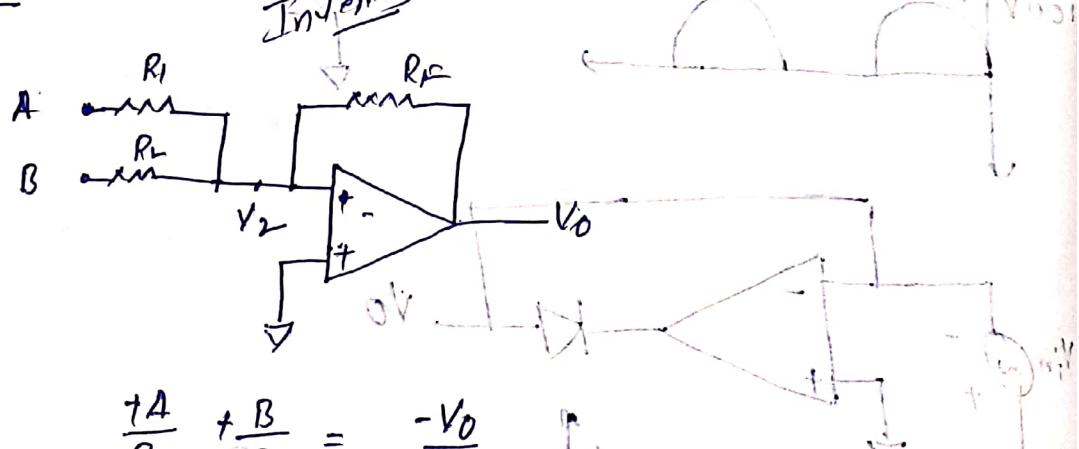


$$\frac{A}{R_1} + \frac{B}{R_2} = \frac{-V_0}{R_F}$$

$$V_0 = -\frac{R_F}{R_1} \left(\frac{A}{R_1} + \frac{B}{R_2} \right)$$


$$R_F = R_1 = R_2$$

fixed weights
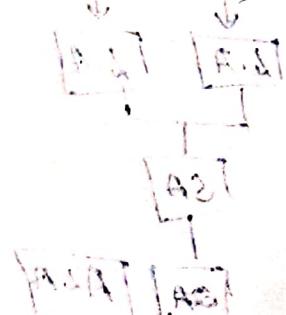
$$\Rightarrow V_0 = -(A + B) \quad \text{fixed weights}$$



Non Inverting

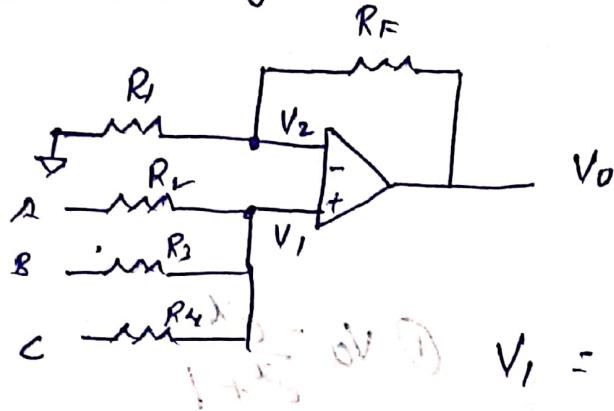

$$V_1 = V_2$$

$$\frac{V_2 - V_0}{R_F} + \frac{V_2}{R_1} = 0$$

$$R_F \left(\frac{V_2}{R_F} + \frac{V_2}{R_1} \right) = V_0$$

$$V_2 = \frac{V_0 R_F R_1}{(R_1 + R_F) R_F}$$

$$\frac{V_1 - V_A}{R_2} + \frac{V_B - V_B}{R_3} + \frac{V_C - V_C}{R_4} = 0$$

$$V_1 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{V_A}{R_2} + \frac{V_B}{R_3} + \frac{V_C}{R_4}$$

$$\frac{V_0 R_1}{R_1 + R_F} \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = \sum V_A R_3 R_4$$

$$V_0 = \frac{(\sum V_A R_3 R_4)(R_1 + R_F)}{(\sum R_2 R_3) R_1}$$

$$R_F = R_2 = R_4$$

$$R_2 = R_3 = R_4$$

Multiplexer

Prakash Patel 1436

$$V_o = K(V_1 + V_2)$$

$$\text{SV} = V \quad \text{① } V_o = \frac{e^x}{e^x + 1}$$

$$\frac{\partial V}{\partial A} = \frac{\partial V}{\partial x} = \frac{\partial V}{\partial A}$$

$$\text{② } V_o = \frac{e^{-x}}{e^x + e^{-x}}$$

$$\frac{\partial V}{\partial A} = \left(\frac{\partial V}{\partial x} + \frac{\partial V}{\partial A} \right) = \frac{\partial V}{\partial x}$$


$$\frac{\partial V}{\partial x} = \frac{\partial V}{\partial A} = \frac{\partial V}{\partial A}$$

$$\frac{\partial V}{\partial A} = \frac{\partial V}{\partial x} + \frac{\partial V}{\partial A} + \frac{\partial V}{\partial A}$$

$$\frac{\partial V}{\partial A} + \frac{\partial V}{\partial A} = \left(\frac{1}{A} + \frac{1}{A} + \frac{1}{A} \right) V$$

$$\left(\frac{1}{A} + \frac{1}{A} + \frac{1}{A} \right) V = \frac{1}{A+1} V$$
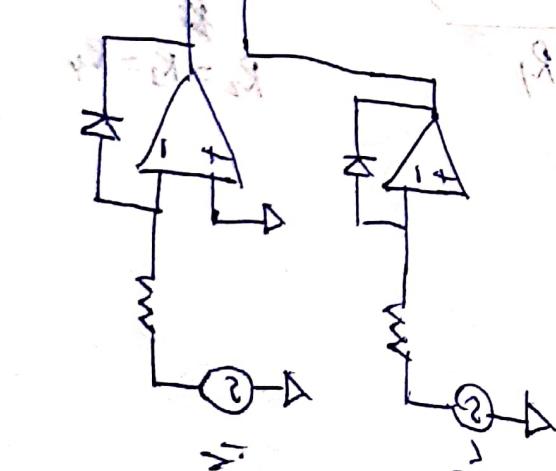
$$\frac{\left(\frac{1}{A} + \frac{1}{A} + \frac{1}{A} \right) V}{A(A+1)} = \frac{1}{A+1} V$$




Dividers:

$$\log(a/b) = \log a - \log b$$

convertors:

Voltage to current converter:

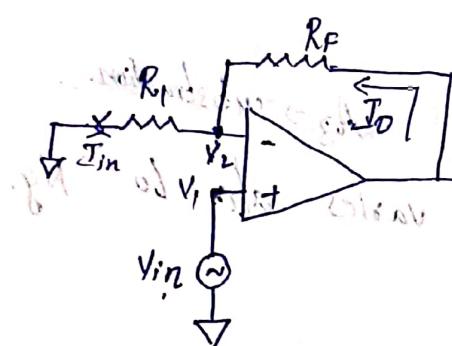


at node V_2

$$I_{in} = I_B \text{ where } I_B = 0$$

$$I_{in} = \frac{V_2 - 0}{R_1} = \frac{V_{in}}{R_1} \quad \text{from } V_G$$

$$I_{in} = \frac{V_{in}}{R_1}$$

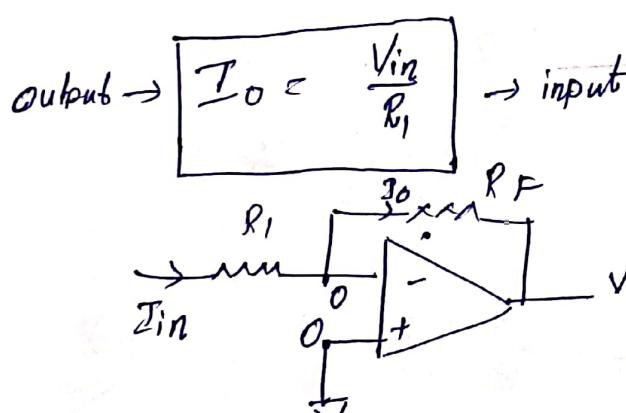


$$\frac{V_O - 0}{R_F} = I_{in}$$

$$V_O = I_{in} R_F$$

Instrumentation Amplifier:

=>

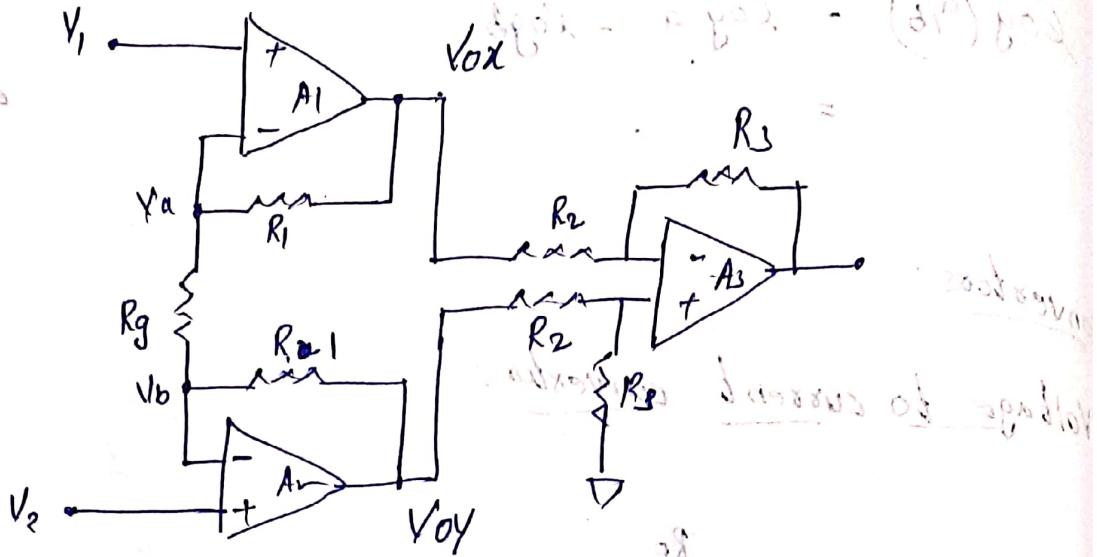

$A_1, A_2 \Rightarrow$ Non-Inverting

\rightarrow very-high gain, gain is varies along R_g .

Case i.


$$V_2 = 0, V_1 \rightarrow V$$



$$\text{at } \frac{\partial V}{\partial I} \text{ mode } \frac{\partial V}{\partial I} = \frac{\partial V}{\partial I}$$

~~Vox~~ = either $A_1 \rightarrow$ Inverting $\frac{\partial V}{\partial I} = \frac{\partial V}{\partial I}$


$A_1 \rightarrow$ Non-Inverting
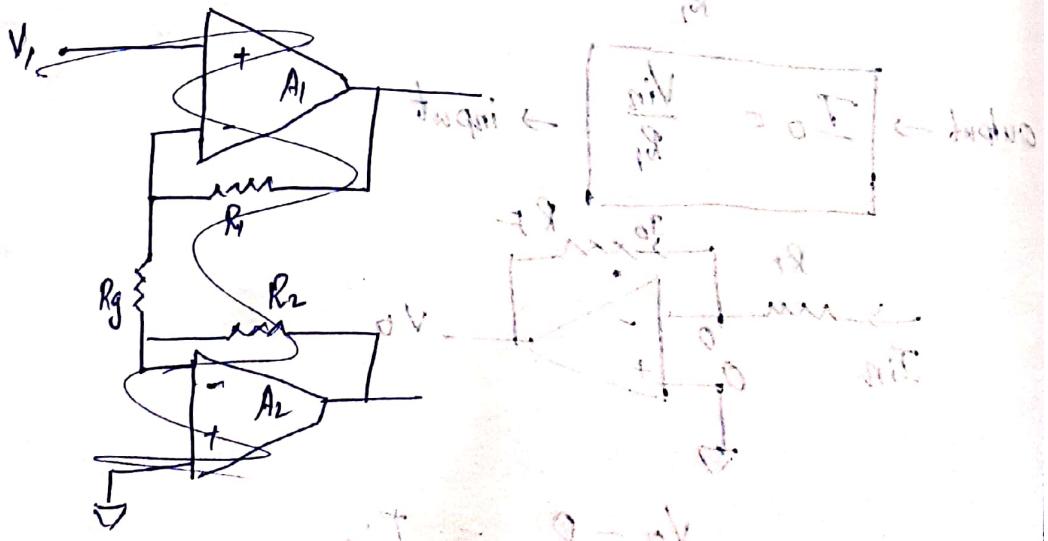
$$\frac{\partial V}{\partial I} = \frac{\partial V}{\partial I}$$



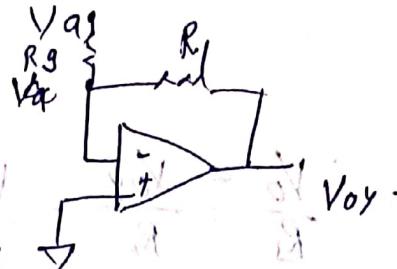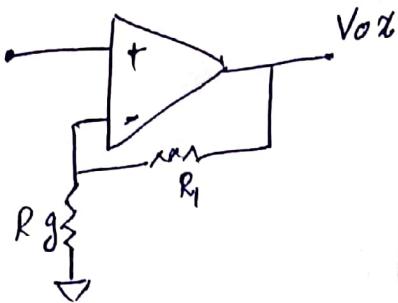
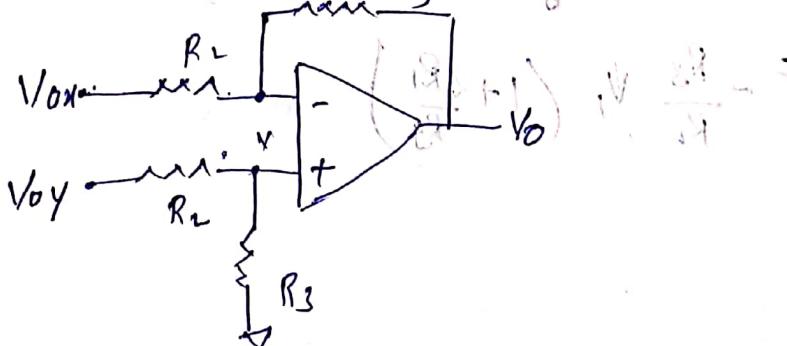
$$V_{ox} = \left(1 + \frac{R_1}{R_g}\right) y, \quad V_{oy} = -\frac{R_1}{R_g} y$$



~~V_o = 0~~

$$\frac{V - V_{ox}}{R_2} + \frac{V - V_o}{R_3} = 0$$

$$V \left(\frac{R_2 + R_3}{R_2 R_3} \right) = \frac{V_{ox}}{R_2} + \frac{V_o}{R_3}$$

$$y = \frac{V_{ox} R_3 + V_o R_2}{R_2 + R_3}$$

$$\frac{V - V_{oy}}{R_2} + \frac{V}{R_3} = 0$$

~~$$\frac{V_{ox}}{R} + \frac{V_o}{R_2} + \frac{V_o R_2}{R_2 + R_3} = \frac{V_{oy}}{R}$$~~

$$\frac{V_{ox} R_3 + V_o R_2 - V_{oy} R_3 - V_{oy} R_2}{R_2} + \frac{V_{ox} R_3 + V_o R_2}{R_3} = 0$$

$$V_o \left(1 + \frac{R_2}{R_3} \right) = V_{oy} \left(\frac{R_3 + R_2}{R_2} \right) - V_{oy} \left(1 + \frac{R_2}{R_3} \right)$$

$$\frac{V_O}{R_2} = \frac{V_{OY}}{R_2} + \frac{V_{OX}}{R_2}$$


$$V_{OY} = \frac{R_3}{R_2} (V_{OY} - V_{OX})$$

$$V_{OY} = \frac{R_3}{R_2} \left(-\frac{R_1}{R_g} V_1 - V_1 - \frac{R_1}{R_g} V_1 \right)$$

$$= -\frac{R_3}{R_2} V_1 \left(1 + \frac{2R_1}{R_g} \right)$$

Case (ii) :

$$V_2 = \dots, \quad V_1 = 0.$$

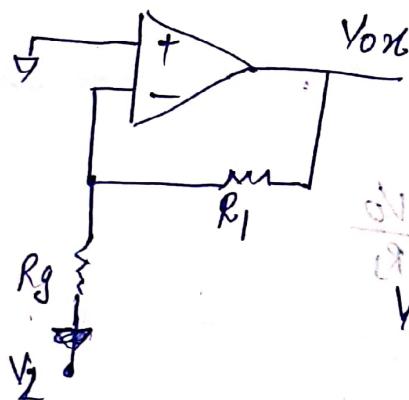

$$V_0 = \frac{AV - V}{R_g} + \frac{AV - V}{R_2}$$

$$V_{OY} = \frac{AV}{R_g} + \frac{AV}{R_2} = \left(\frac{A+2}{R_g} \right) V$$

$$V_{OY} = \left(1 + \frac{R_1}{R_g} \right) V_2$$

$$V_{OY} = \frac{R_3}{R_2} V_2 \left(1 + \frac{2R_1}{R_g} \right)$$

$$V_{OY} = \frac{R_3}{R_2} V_2 \left(1 + \frac{2R_1}{R_g} \right) + \frac{R_3}{R_2} V_2 \left(1 + \frac{2R_1}{R_g} \right) + \dots$$

Final Answer : $(V_{OY} = V_2 \left(1 + \frac{2R_1}{R_g} \right))$

$$V_o = V_{o1} + V_{o2} + V_{o3}$$


$$V_o = \frac{R_3}{R_2} \left(1 + \frac{2R_1}{R_g} \right) (V_2 - V_1)$$

$$\text{Gain} = \frac{V_o}{V_2 - V_1} = \frac{R_3}{R_2} \left(1 + \frac{2R_1}{R_g} \right)$$

$$\text{ii}) \quad \frac{dx}{dy} - 5x = 0$$

$$\frac{dx}{dy} = 5x$$




$$dx = 5x dy$$

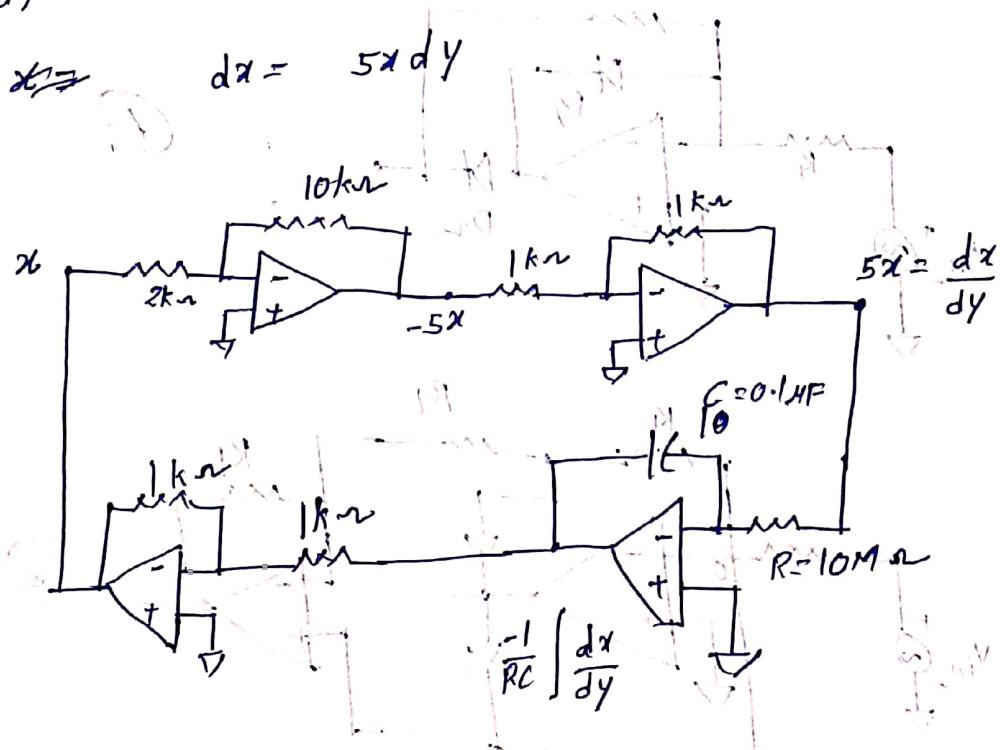

$$\text{i)} \quad \frac{dx^2}{dy^2} - 10 \frac{dx}{dy} + 5x = 0 \quad (3)$$

$$\text{ii)} \quad \frac{dx^2}{dy^2} + 15 \frac{dx}{dy} - 10x = 0 \quad (4)$$

iii)

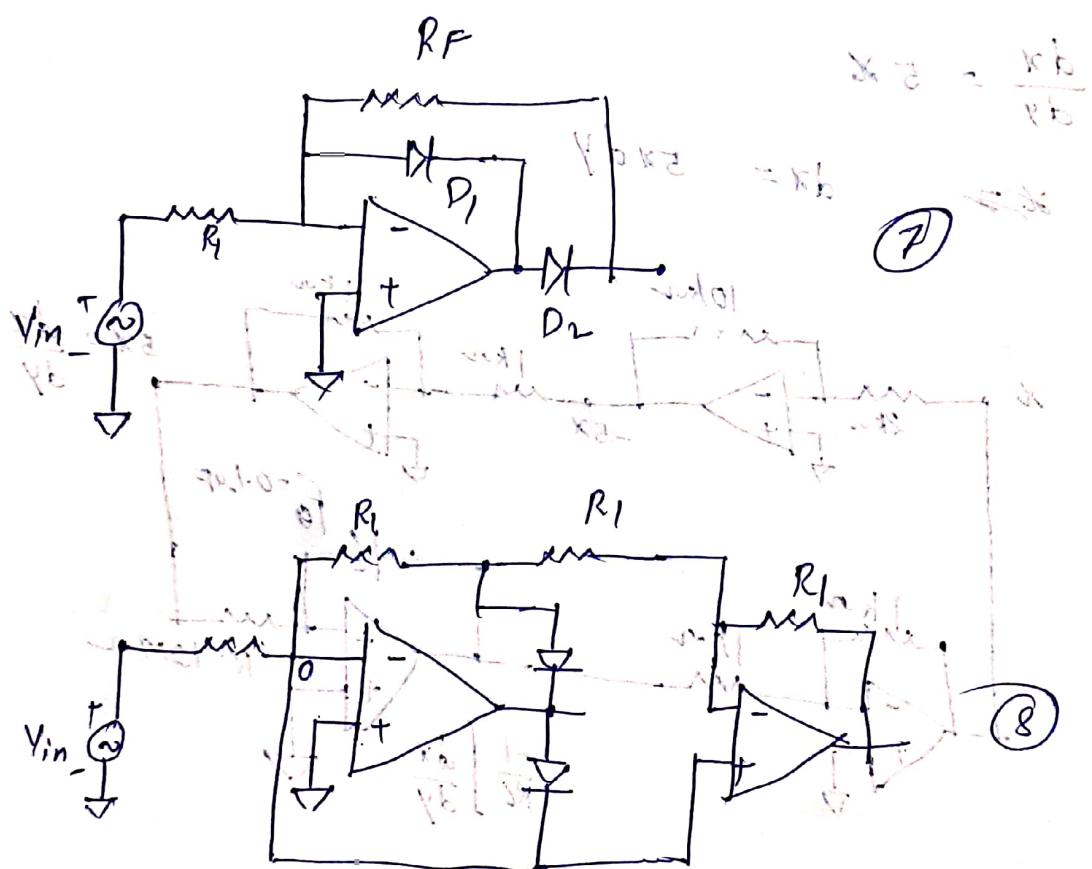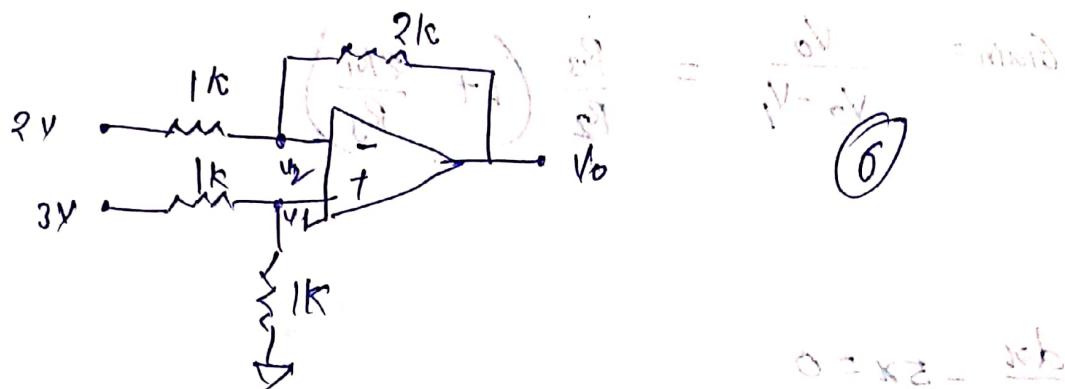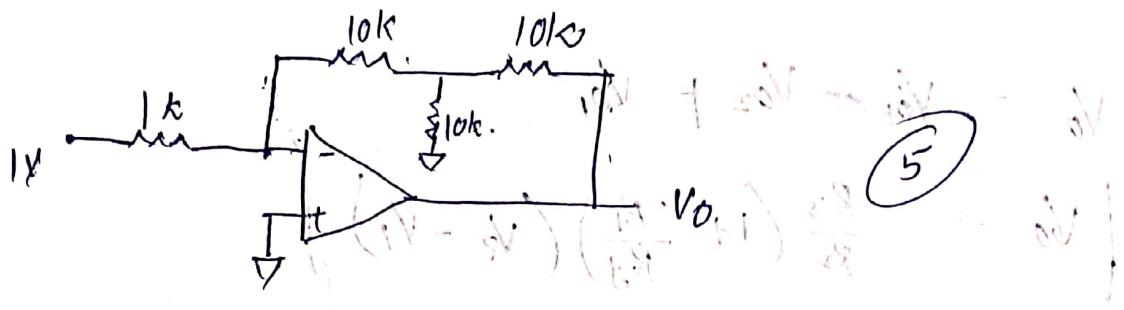

$$\frac{dx^2}{dy^2} - \frac{10}{dy} \frac{dx}{dy} + 5x = 0$$

$$V_1 = -3 + V_1 = 0$$


$$V_1 = \frac{3}{2} = V_2$$

$$\frac{\frac{3}{2} - 2}{(1.5)} + \frac{\frac{3}{2} - V_0}{2} = 0$$

$$(1.5) \cdot \frac{3}{2} - V_0 = 1$$

$$V_0 = \frac{3}{2} - 1 \\ = 0.5$$

Frequency response of OP-Amp :-

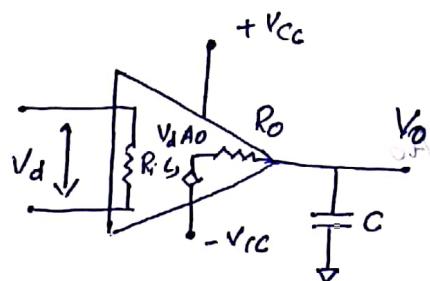


Equivalent circuit of op-amp

R_i - input Resistance

R_o - output Resistance

C - load capacitance.

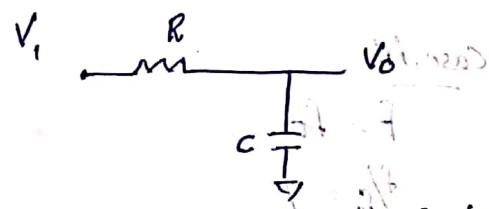

$$V_o = \left(\frac{Y_{SC}}{R + Y_{SC}} \right) V_d A_o$$

$$Y_o = \left(\frac{1}{1 + sCR} \right) V_d A_o$$

$$= \left(\frac{1}{1 + 2\pi f CR} \right) V_d A_o$$

$$V_o = \left(\frac{Y_{SC}}{R + Y_{SC}} \right) V_i \quad s = j\omega$$

$$\text{Gain} \Rightarrow \frac{V_o}{V_d} = \frac{A_o}{1 + 2\pi f CR}$$

Let $f_0 = \frac{1}{2\pi CR} \Rightarrow$ Depended on the
components.

$$\frac{V_o}{V_d} = \left(\frac{A_0}{1 + j f/f_0} \right)$$


$$\begin{aligned} \left| \frac{V_o}{V_d} \right| &= \frac{A_0}{\sqrt{1 + (f/f_0)^2}} \quad N = 2^8 = 256 \\ &= \frac{A_0}{\sqrt{1 + (f/f_0)^2}} \quad \theta = \tan^{-1} \left(-\frac{f/f_0}{1} \right) \\ &\quad 1 - \frac{f}{f_0} = \tan^{-1} \left(\frac{f/f_0}{1} \right) \end{aligned}$$

Case i.:

$$f \ll f_0$$

$$\begin{aligned} f/f_0 &<< 1 \quad \text{neglect } f/f_0 \text{ terms} \\ f_0 &\text{ neglecting } f/f_0 \text{ terms} \end{aligned}$$

$$\left| \frac{V_o}{V_d} \right| = \frac{A_0}{\sqrt{1}} = A_0$$

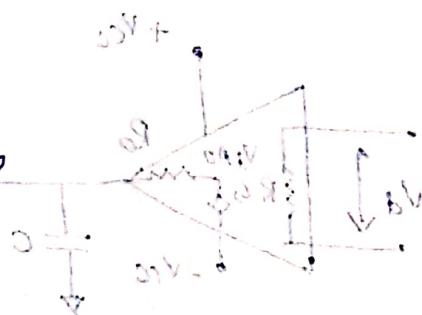

Case ii.:

$$f = f_0$$

$$f/f_0 = 1$$

$$\left| \frac{V_o}{V_d} \right| \approx \left(\frac{A_0}{\sqrt{2}} \right)$$

Circuit diagram (neglect - 2)


$$\left| \frac{V_o}{V_d} \right| = \left(\frac{A_0}{\sqrt{1 + 1}} \right) \sqrt{\frac{f_0}{f}}$$

$$\left(\frac{A_0}{\sqrt{2}} \right) \frac{f_0}{f} \sqrt{2}$$

$$\text{Ansatz: } \frac{dV}{dN} = \infty$$

$$\left(\frac{A_0}{\sqrt{2}} \right) \frac{f_0}{f} \sqrt{2}$$


frequency Vs Gain :-

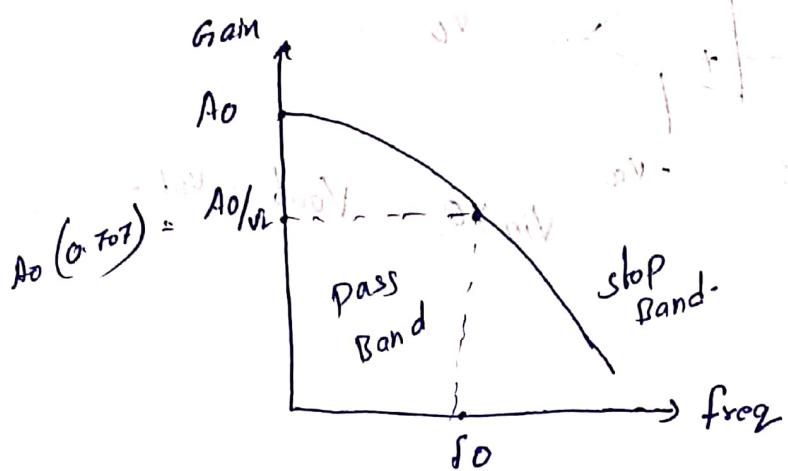

- Allowing low freq.
- Power calculated by at $A_0/\sqrt{2}$
- Op-Amp acts as low-pass filter.
- At pass Band it allows freqies.
- At stop Band it stops "

Comparators :-

open loop

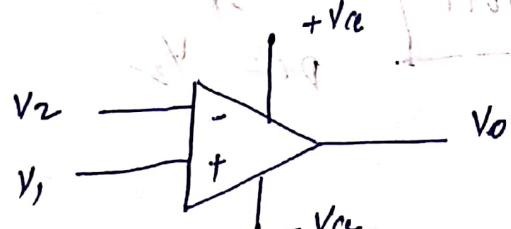





$$V_1 > V_2 \rightarrow V_0 = +V_{cc} / +V_{sat}$$

$$V_1 < V_2 \rightarrow V_0 = -V_{cc} / -V_{sat}$$

→ converter Analog to digital.

inverting

zero crossing
detector.

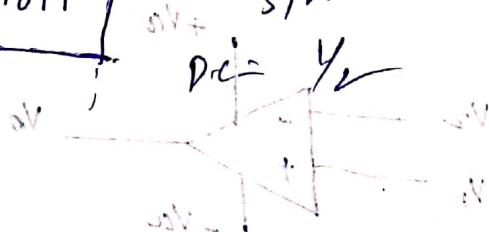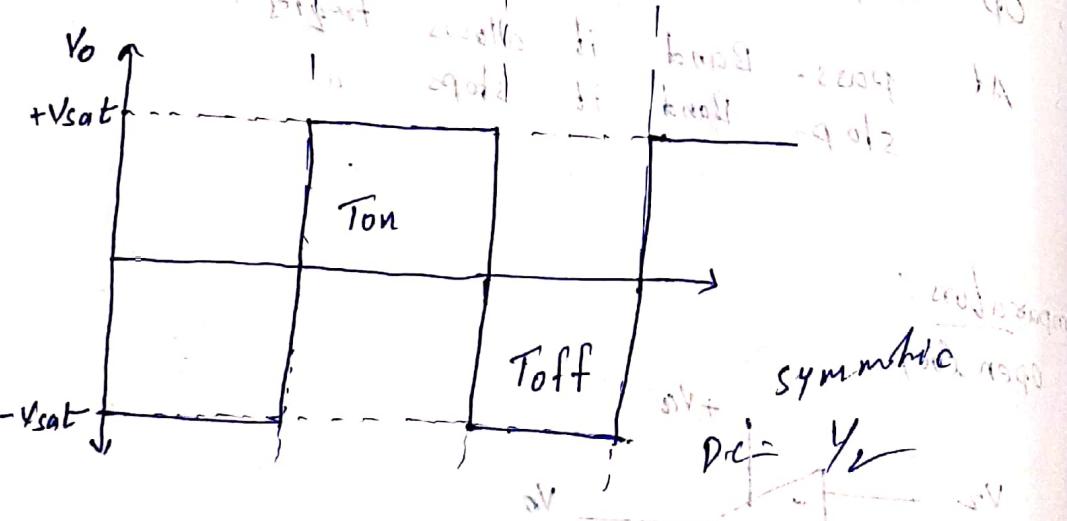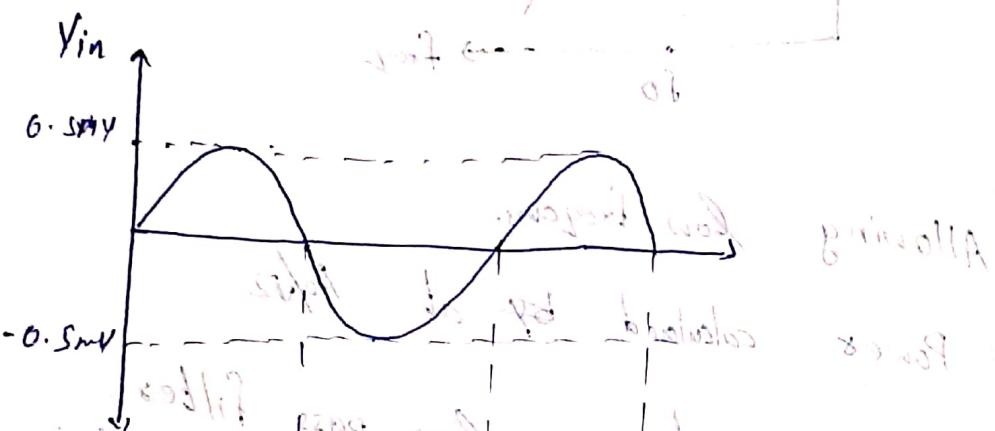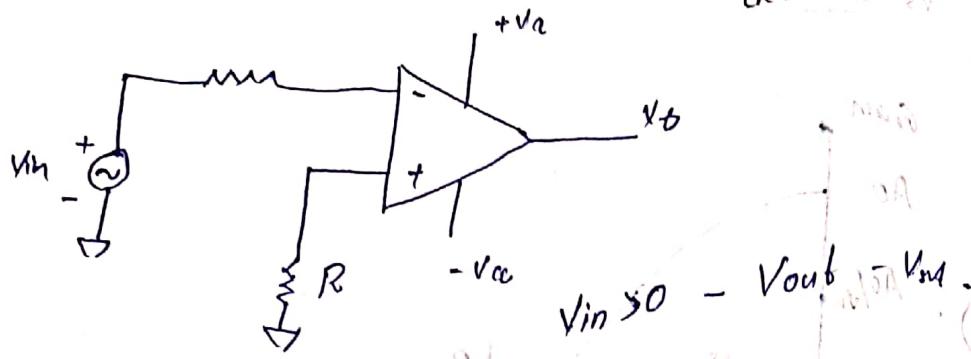

sinoidal \rightarrow square.


characteristics:

i) high speed


ii) accuracy.


iii) Output is comparable.

Non-inverting

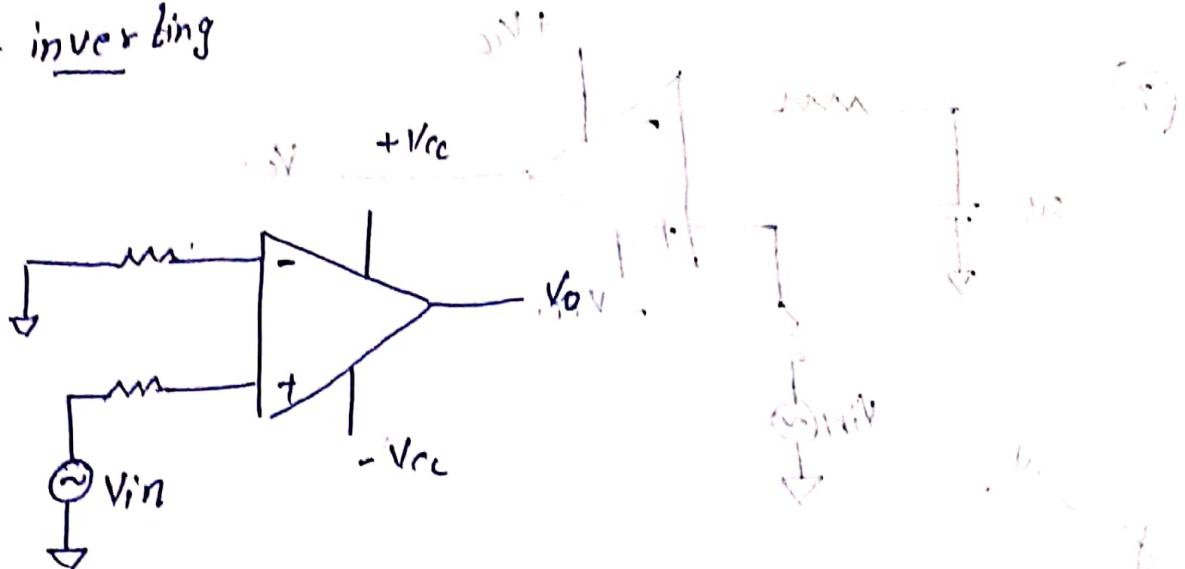


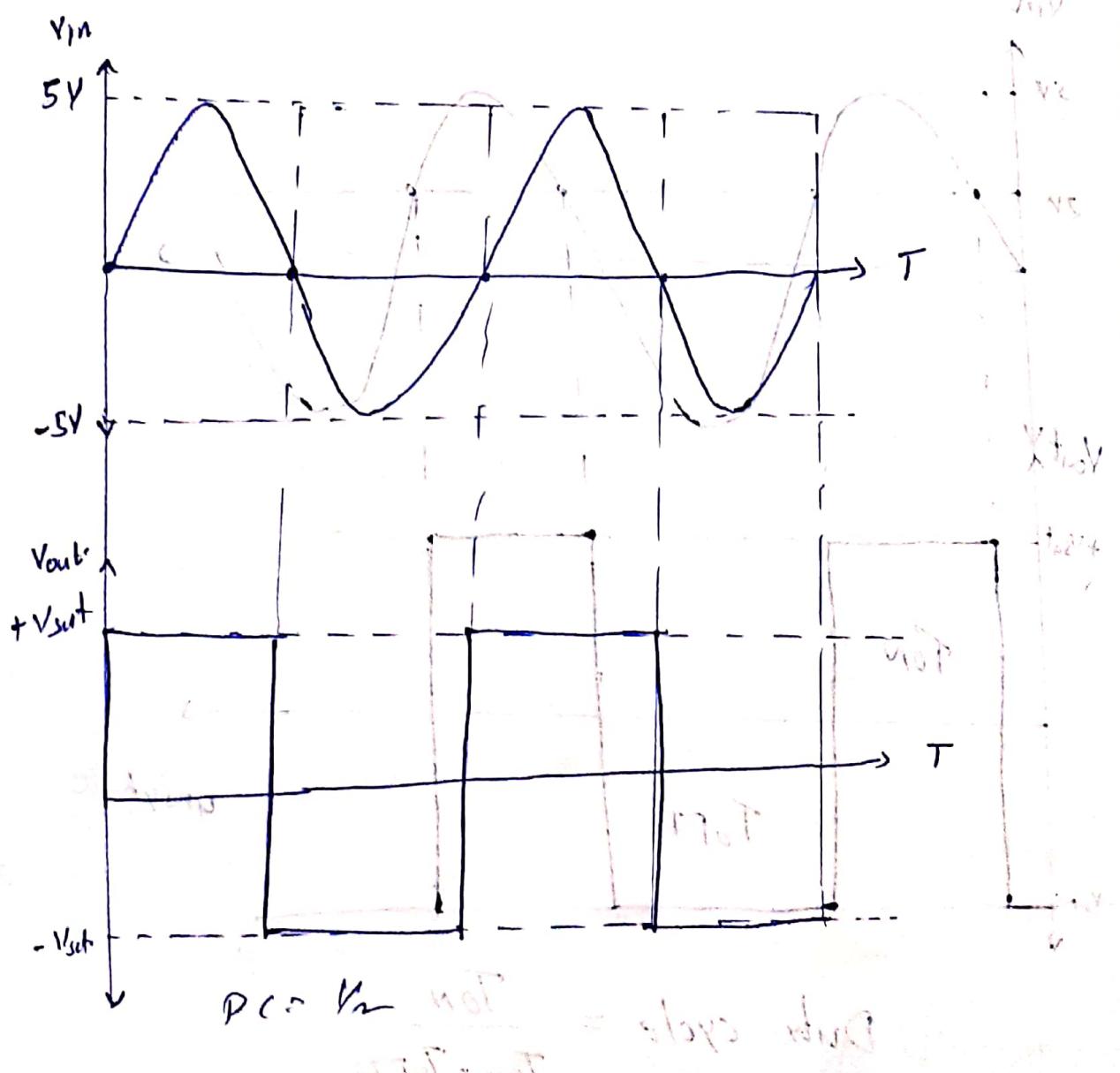$V_{in} > 0 \rightarrow V_{out} = V_{in} + V_{cc}$
 $V_{in} < 0 \rightarrow V_{out} = V_{in} - V_{ee}$



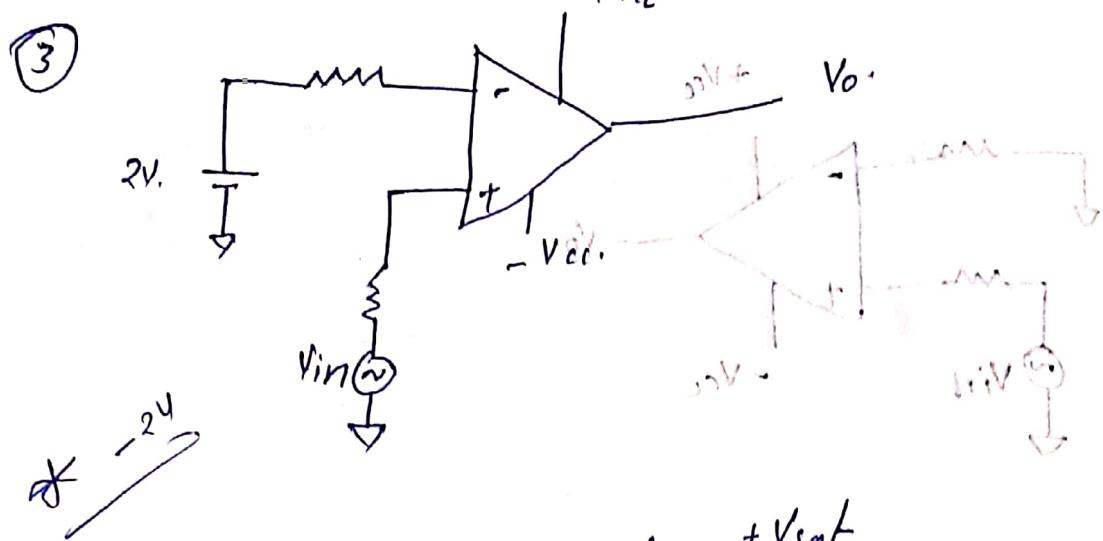

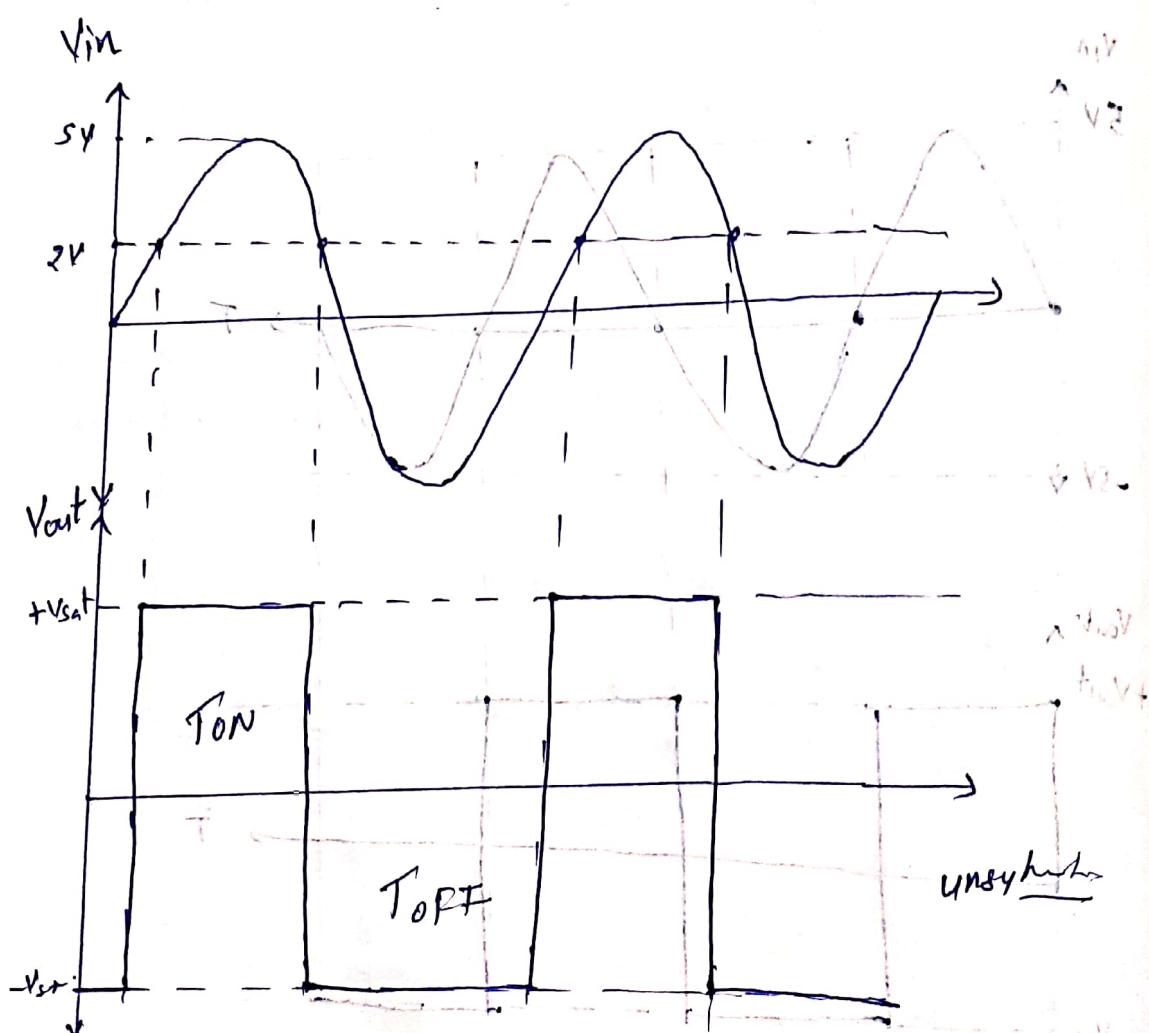
$$\begin{aligned} & \text{if } V_{in} > 2V \quad V_{out} = +V_{sat} \\ & \text{if } V_{in} < -2V \quad V_{out} = -V_{sat} \end{aligned}$$



$$\text{Duty cycle} = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

Schmitt Trigger :-

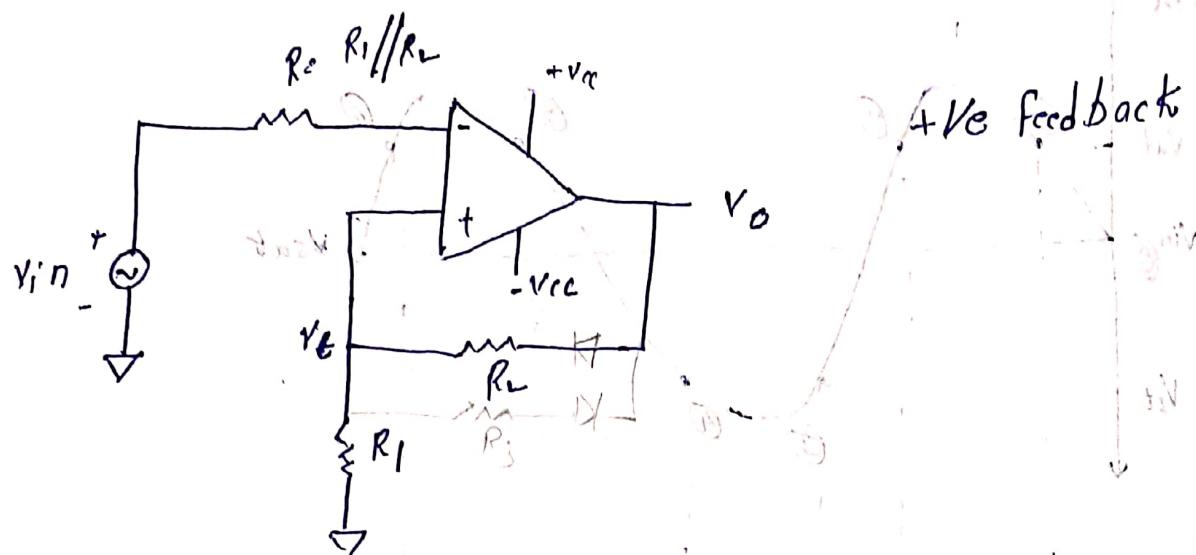

$$\frac{V_t}{R_1} + \frac{V_t - V_0}{R_2} = 0.$$

$$V_t = \frac{V_0}{R_2} \left(\frac{R_1 R_2}{R_1 + R_2} \right).$$

$$= \frac{V_0 \cdot R_1}{R_1 + R_2}$$

$$V_0 + V_{cc} \rightarrow V_t - \text{upper threshold} = V_{ut}$$

$$V_0 - V_{cc} \rightarrow V_t - \text{lower threshold} = V_{lt}$$


Case i)

$$V_{in} > V_t \Rightarrow V_0 = -V_{sat}$$

Case ii)

$$V_{in} < V_t \Rightarrow V_0 = +V_{sat}$$
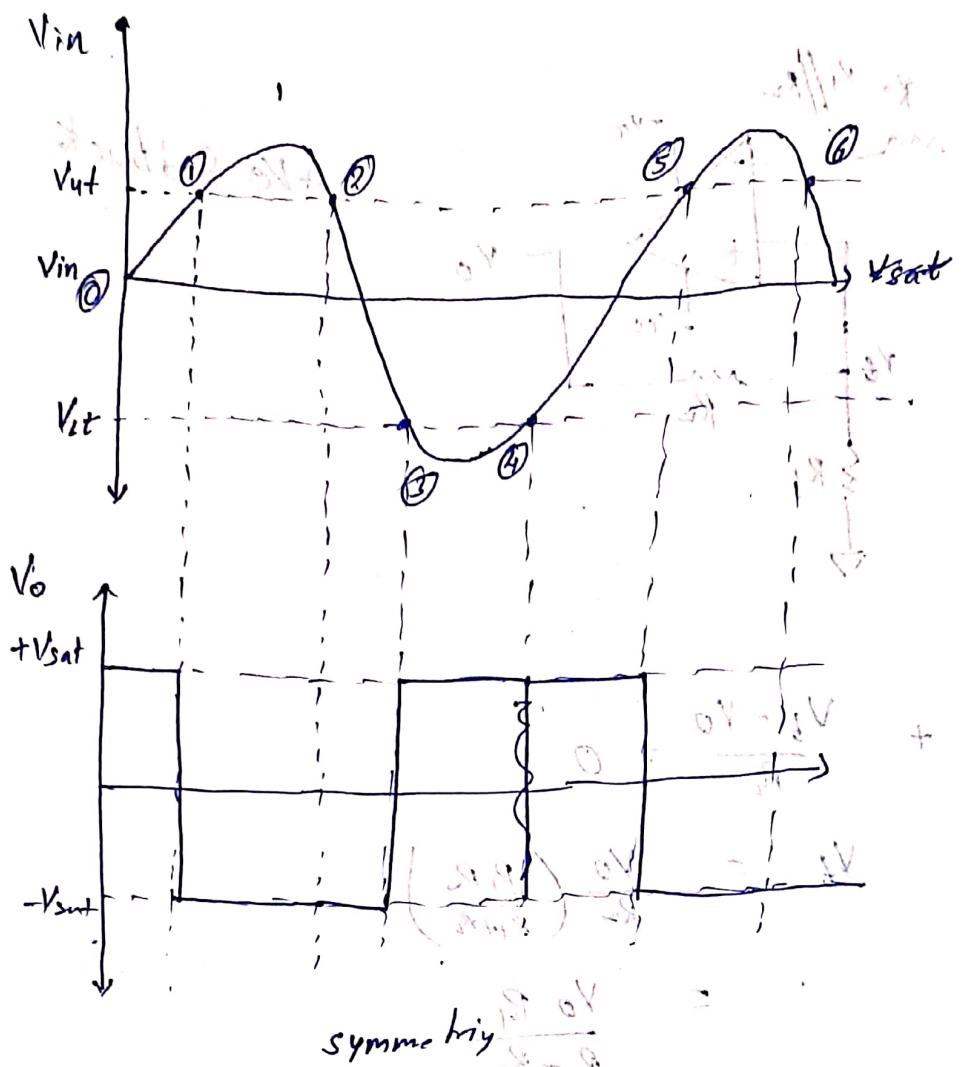
$$V_{ut} = \left(\frac{R_1}{R_1 + R_2} \right) (V_{sat}) \quad V_{lt} = \left(\frac{R_1}{R_1 + R_2} \right) (-V_{sat})$$



Duty cycle = 50%

0 to 1

$$V_{in} < V_{ut} \Rightarrow V_o = +V_{sat}$$

\Downarrow

$$V_t = V_{ut}$$

1 to 2 $V_t = V_{ut}$

$$V_{in} > V_{ut} \Rightarrow V_o = -V_{sat}$$

\Downarrow

$$V_t = V_{ut}$$

2 to 3 $V_t = V_{ut}$

$$V_{in} > V_{ut} \Rightarrow V_o = -V_{sat}$$

\Downarrow

$$V_t = V_{ut}$$

$$\frac{3 to 4}{3 to 4} V_t = V_{ut}$$

$$V_{in} < V_{ut} \Rightarrow V_o = +V_{sat}$$

\Downarrow

$$V_t = V_{ut}$$

4 to 5

$$V_t = V_{ut}$$

$$V_{in} < V_{ut} \Rightarrow V_o = +V_{sat}$$

$$\frac{5 to 6}{5 to 6} V_t = V_{ut}$$


$$V_{in} > V_{ut} \Rightarrow V_o = -V_{sat}$$

$$V_t = V_{ut}$$

Hysteresis curr:-

$$V_{HY} = V_{ut} - V_{st}$$


Dead zone

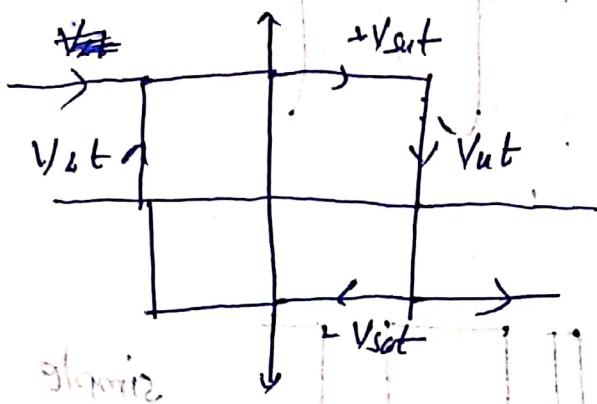


→ To determine the unknown current (or) voltage by known values by using comparators.

→ Applications :- of comparators:

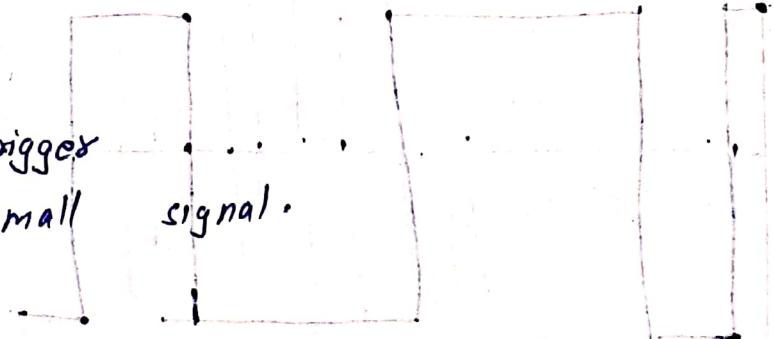
- i) analog → digital.
- ii) switch
- iii) zero crossing trigger
- iv) identify the small signal.



⇒

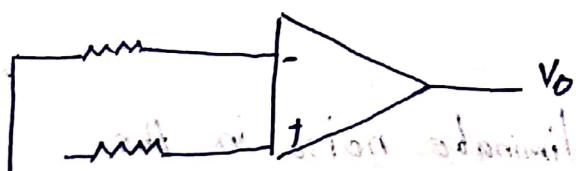


non inverting op-amp as basic switching

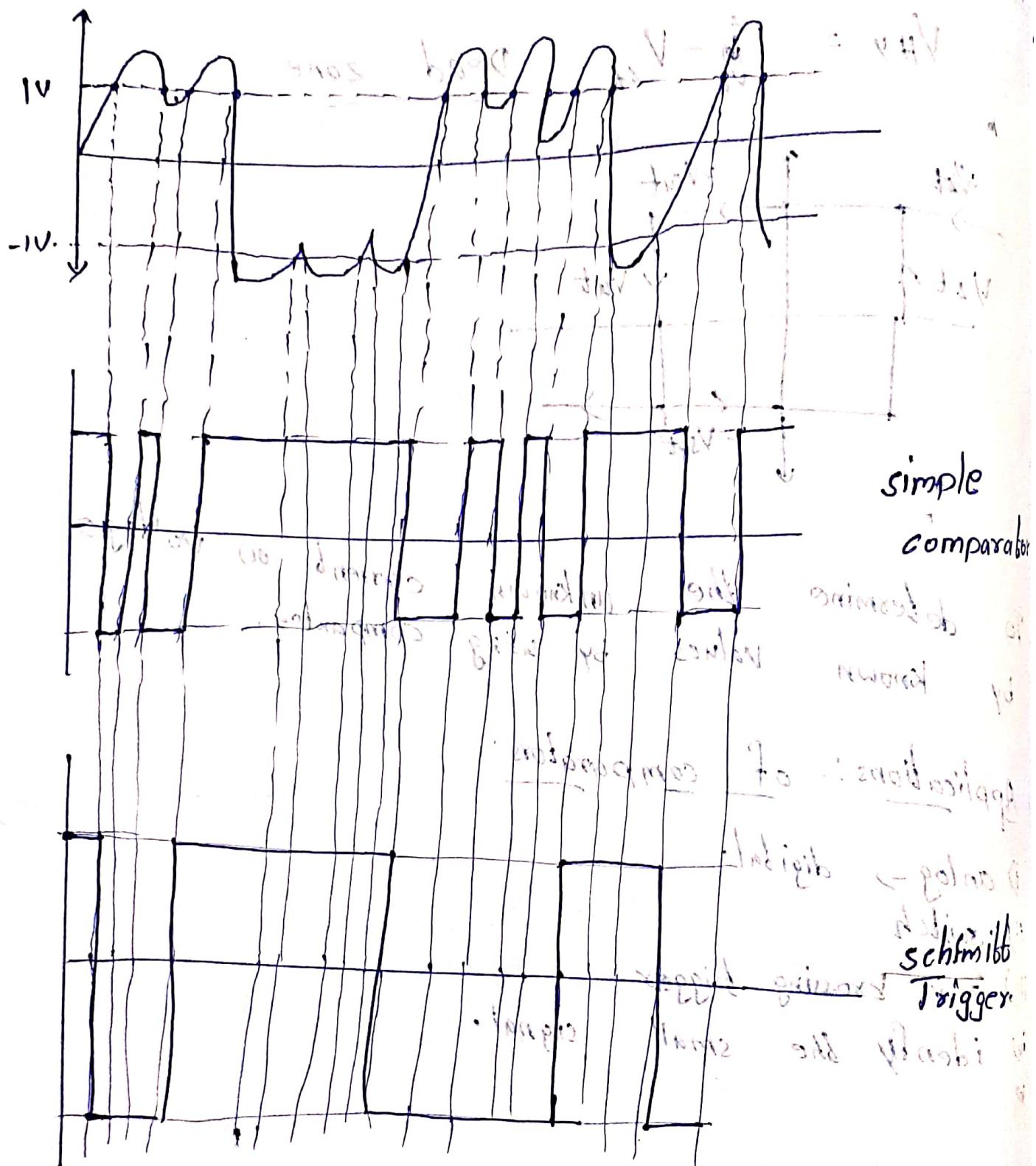


⇒ This used to eliminate noise in the Output wave.

Q9) Design a comparitor with two threshold lines which are not equal.

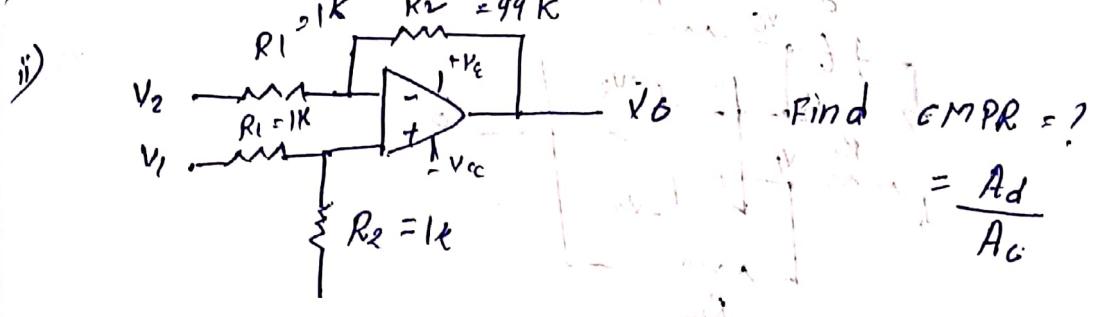Q10) Design a non-inverting schmitt trigger.



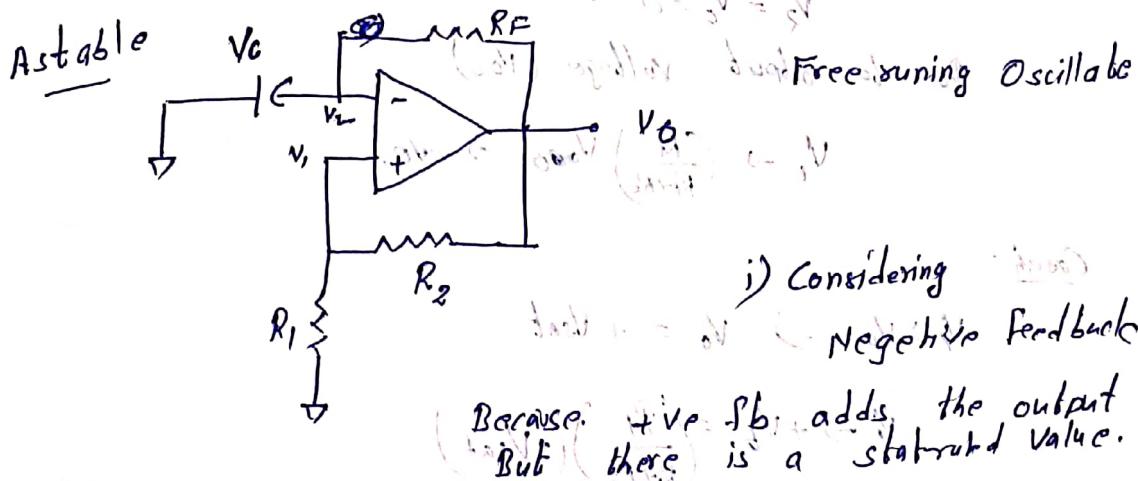Multivibrator:
 i) Asstable ✓
 ii) Monostable ✓
 iii) Bi-stable ✗



$$\nabla \rightarrow V_2 \rightarrow$$

$$i) V_1 > V_2 \rightarrow V_0 = +V_{sat}$$

$$ii) V_1 < V_2 \rightarrow V_0 = -V_{sat}$$

$$\text{at } t=0, V_C = 0 \quad \text{Offset voltage}$$

$$V_C = V_2 \cdot \frac{1}{1 + \frac{R_1}{R_2}} = \left(\frac{R_1}{R_1 + R_2} \right) V_{00}$$


$$V_1 > V_2 \Rightarrow V_0 = +V_{sat}$$

\Rightarrow Capacitance charging

If this charging more than V_1 ,

$$\Rightarrow V_C > V_1 \Rightarrow V_0 = +V_{sat}$$

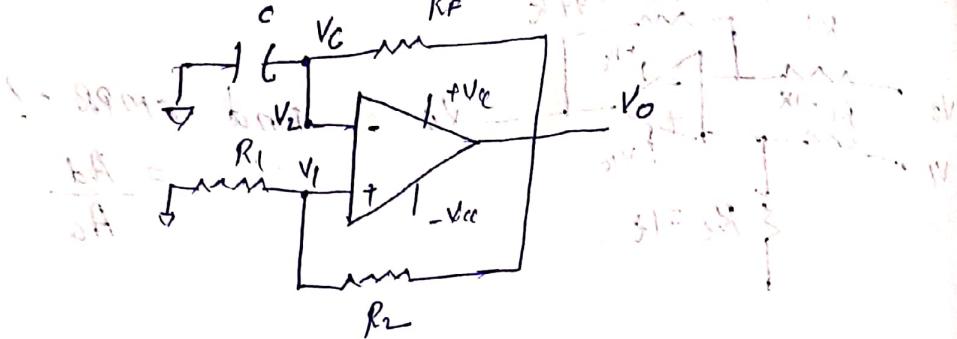\Rightarrow Capacitance discharges. \Rightarrow Then continues



at $t=0 \quad V_C = 0$

$$V_2 = V_C = 0$$

Due to V_2 output voltage (V_{out})

$$V_1 \rightarrow \left(\frac{R_1}{R_1 + R_2} \right) V_{out} \Rightarrow +V_{sat}$$

Case I:

$$\text{if } V_1 > V_{sat} \Rightarrow V_0 = +V_{sat}$$

$$\text{when } V_2 > V_1 \Rightarrow +V_2 = \left(\frac{R_1}{R_1 + R_2} \right) (+V_{sat})$$

$$\text{when, } V_0 = +V_{sat}$$

$V_C \rightarrow$ charge through R_F

Case II: when

$$V_1 < V_{sat}$$

$$\text{and } \left(\frac{R_1}{R_1 + R_2} \right) V_1 = -V_2 \Rightarrow \left(\frac{R_1}{R_1 + R_2} \right) = -V_{sat}$$

$$V_C > V_0 \Rightarrow V_C < V$$


$V_C \rightarrow$ discharge through R_F

Case III:

when, $V_1 = V_{sat}$

$$V_2 < V_1 \Rightarrow V_0 = +V_{sat}$$
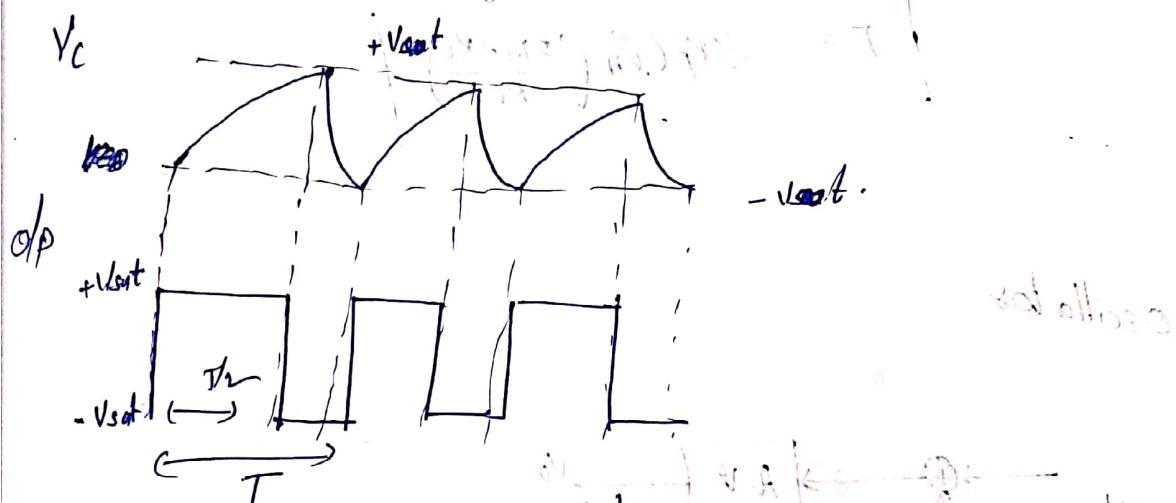
$$V_1 = +V_2 = \left(\frac{R_1}{R_1 + R_2} \right) (+V_{sat})$$



$$V_C = V_0 \left(1 - e^{-t/\tau} \right) \quad \text{charging}$$

$$V_C = V_0 e^{-t/\tau} \quad \text{discharging}$$

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t/\tau}$$

$$= +V_{sat} + \left[\left(\frac{-R_1}{R_1 + R_2} \right) V_{sat} - V_{sat} \right] e^{-t/\tau}$$

$$\tau = T/2$$

$$\tau = RC = \frac{R_F C}{-T/2 R_G}$$

$$e^{-t/\tau} = e^{\frac{t}{\tau}}$$

$$\left(\frac{R_1}{R_1 + R_2} \right) V_{sat} = V_{sat} - \left(\left(\frac{R_1}{R_1 + R_2} \right) V_{sat} + V_{sat} \right) e^{-t/\tau}$$

$$\frac{R_1}{R_1+R_2} = 1 - \left(\frac{2R_1 + R_2}{R_1 + R_2} \right) e^{-T/2R_F C}$$


$$(2R_1 + R_2) e^{-T/2R_F C} = R_2$$

$$e^{T/2R_F C} = \frac{2R_1 + R_L}{R_2}$$

$$\frac{T}{2R_F C} = \log \left(\frac{2R_1 + R_L}{R_2} \right)$$

$$\boxed{T = \frac{2R_F C \log}{2R_F C \ln \left(\frac{2R_1 + R_L}{R_2} \right)}}$$

oscillators

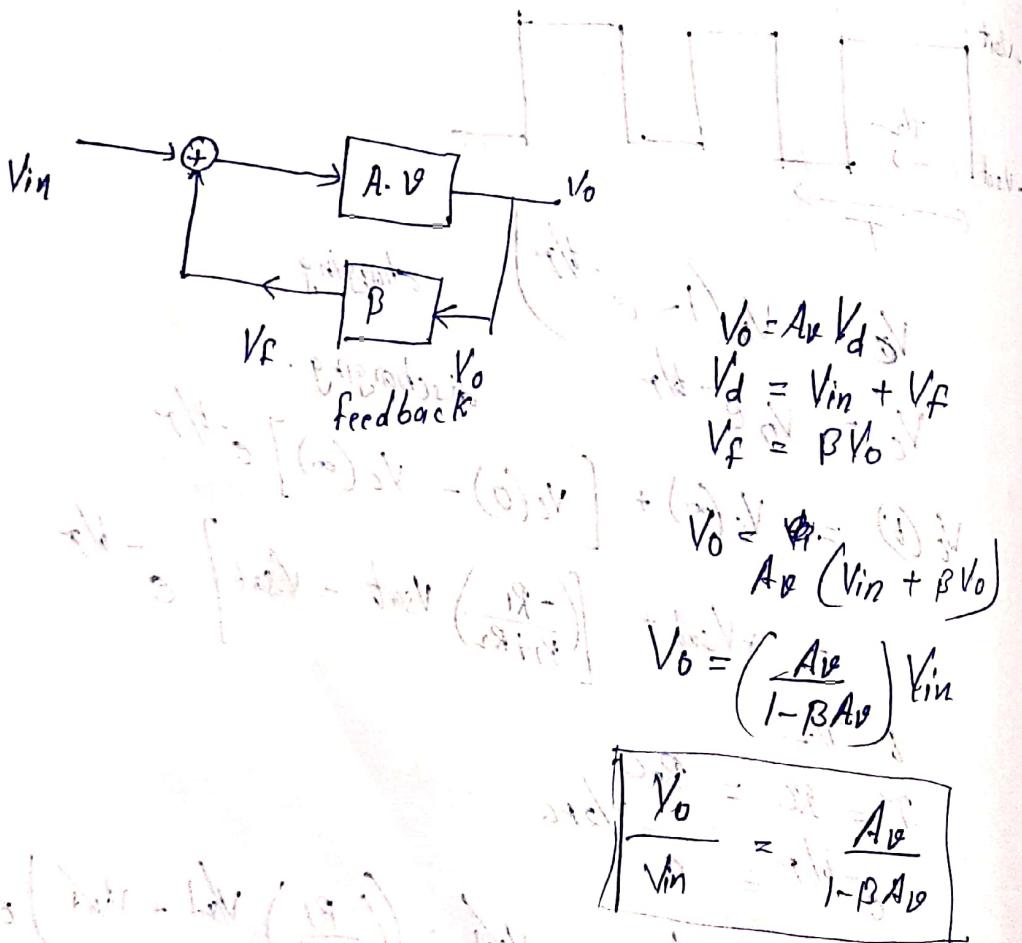

$$V_{in} = 0 \Rightarrow V_o \neq 0$$

$$1 - A_v \beta = 0$$

$$\boxed{A_v \beta = 1}$$

polar form


Total loop gain $= 1$

$$A_v \beta = 1 \text{ Lo. } \angle A_v \beta = 0^\circ \text{ (at) } 360^\circ$$

Barkhausen stability criterion:

i) $A_v \beta = 1$

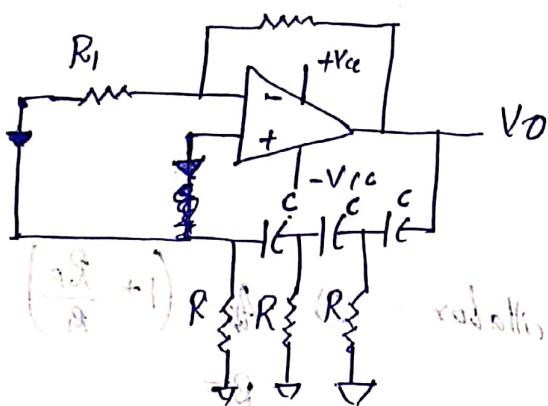ii) phase angle $= 0^\circ \text{ (at) } 360^\circ$



$\theta = 60^\circ$ for $1RC$ combination
For -ve feedback $\approx 180^\circ$ phase

$$+ve \rightarrow 3 \times RC \approx 360^\circ$$

$= 180^\circ$ phase

Total 360°


$$A_v \beta = 1$$

$$A_v = \frac{-R_F}{R_1}$$

β

$$\boxed{\frac{R_F}{R_1} = 29}$$

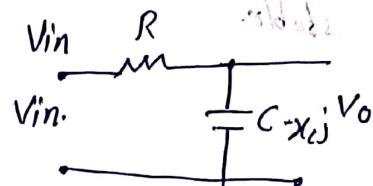
$$f = \frac{1}{2\pi\sqrt{6}RC} \sqrt{2N}$$





$$\begin{aligned} * & R + jX_C \\ \frac{V_{in}}{V_o} &= \frac{R}{R+jX_C} \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} e^{-j\arctan(X_C/R)} \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} \left(\cos(-\arctan(X_C/R)) - j \sin(-\arctan(X_C/R)) \right) \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} \left(\frac{R}{\sqrt{R^2 + X_C^2}} - j \frac{X_C}{\sqrt{R^2 + X_C^2}} \right) \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} \left(\frac{R^2 - X_C^2}{R^2 + X_C^2} - j \frac{2RX_C}{R^2 + X_C^2} \right) \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} \left(\frac{R^2 - X_C^2}{R^2 + X_C^2} - j \frac{2RX_C}{R^2 + X_C^2} \right) \\ &= \frac{R}{\sqrt{R^2 + X_C^2}} \left(\frac{R^2 - X_C^2}{R^2 + X_C^2} - j \frac{2RX_C}{R^2 + X_C^2} \right) \end{aligned}$$

Pg 527

Wien Bridge oscillator

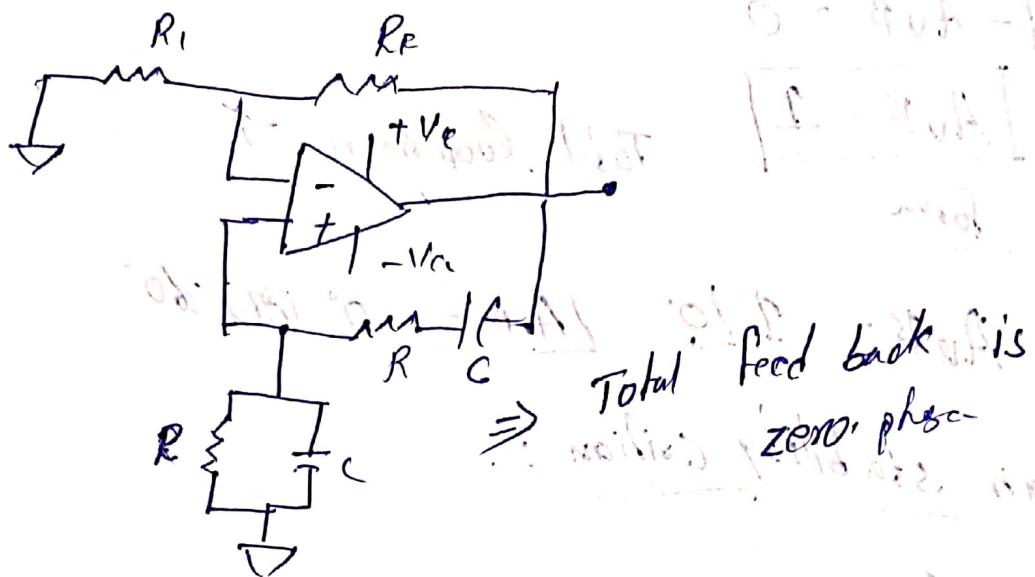


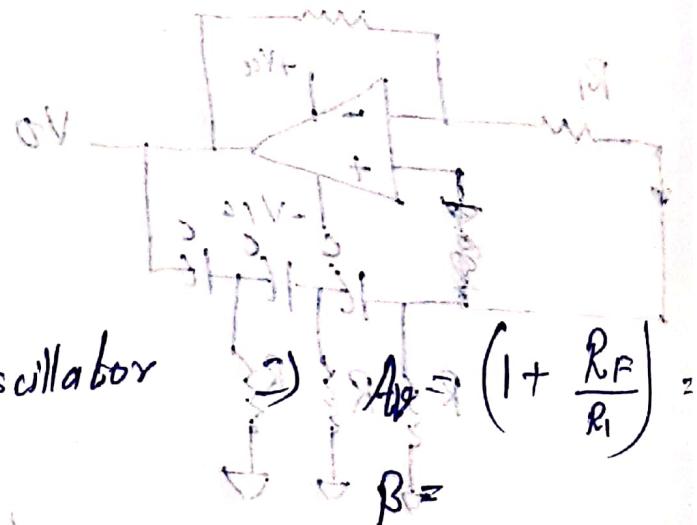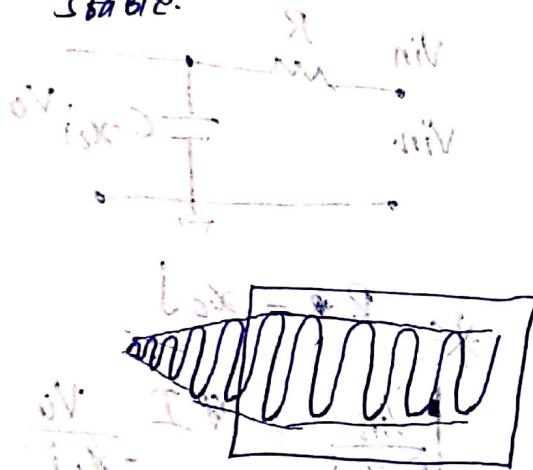- The input is given by noise of CR_1C_2 .
- This noise is kept on adding - Then it becomes stable.



$$f = \frac{1}{2\pi R C}$$

- | <u>RC phase shift</u> | <u>Wcm Brdg.</u> |
|---------------------------|--------------------------|
| i) Negative feedback. | j) +ve. feedback. |
| ii) less frequency | ii) more frequency |
| iii) limited frequencies. | iii) Variable frequency. |
| iv) complex circuit | iv) simple circuit |
| v) phase diffrc 280° | v) phase diffrc 0° |

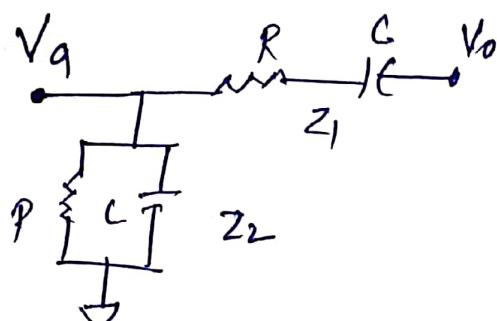

$$\beta = \frac{V_a}{V_o}$$

$$Z_1 = R - X_C j$$

$$= R + Y_{SC} = \frac{R_{SC} + 1}{SC}$$

$$Z_2 = \frac{R Y_{SC}}{R + Y_{SC}} = \frac{R}{R_{SC} + 1}$$

$$\frac{V_o - 0}{Z_2} = + \frac{V_a - V_o}{R + Y_{SC}}$$

$$\frac{V_a}{Z_2} = - \frac{V_a - V_o}{Z_1}$$

$$- \frac{Z_1}{Z_2} V_a = V_a - V_o$$

$$V_o = V_a \left(1 + \frac{Z_1}{Z_2} \right)$$

$$\frac{V_o}{V_a} = \frac{Z_2 + Z_1}{Z_2}$$

$$\beta = \frac{Z_2}{Z_2 + Z_1}$$

$$= \frac{\frac{R}{R_{SC} + 1}}{\frac{R_{SC} + 1}{R_{SC}} + \left(\frac{R_{SC} + 1}{R_{SC}} \right)^2}$$

~~$$= \frac{R_{SC}}{(R_{SC})^2 - 1 - R_{SC}}$$~~

$$= \frac{R_{SC}}{R_{SC} + (R_{SC} + 1)}$$

2nd year

High frequency

$$A_V \approx 1 + \frac{R_F}{R_I} \text{ (for } R_F \gg R_I)$$

$$\left(1 + \frac{R_F}{R_I}\right)^2 \left(\frac{2\pi R_C S}{(R_C S + 1)^2 R_C S} \right) = 1$$

$$\left(1 + \frac{R_F}{R_I}\right) j R_C \omega \approx -R_C^2 \omega^2 + j 2 R_C \omega + f$$

$$2 R_C \omega \approx R_C \omega \left(1 + \frac{R_F}{R_I}\right)$$

$$A_V \approx 1 + \frac{R_F}{R_I} = 1$$

$$R_F = 2 R_I$$

$$j \omega L = R_C^2 \omega^2$$

$$\frac{j \omega L}{1 + j \omega L} = \frac{j \omega L}{1 + j \omega L}$$


$$f_2 = \frac{1}{2\pi R_C \omega} = \frac{1}{2\pi R_C}$$

$$\frac{1}{f_2} = \frac{1}{2\pi R_C}$$

$$f_{22} = \frac{1}{2\pi R_C}$$

$$f_{22} = \frac{1}{2\pi R_C}$$

22

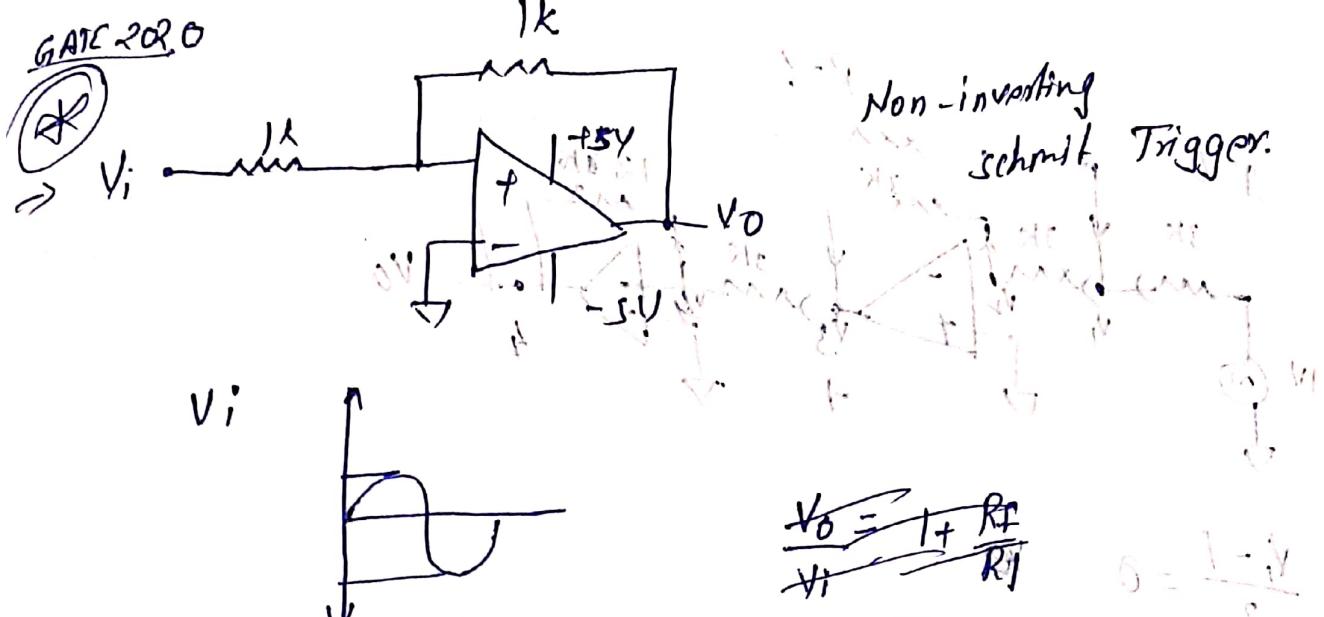

→ straight line.

→

$\frac{V_o - 10}{10} + \frac{V_o - V_2}{100} = 0$

$10V - 100V + 10V_o = 0$

$10V_o = 80V$

$V_o = 8V$

$\frac{V_o - 50}{10} + \frac{V_o - V_2}{100} = 0$

$50V - 100V + 10V_o = 0$

$10V_o = 50V$


$V_o = 5V$

$10V_o = 100V + 10V$

$90V_o = 110V$

$V_o = 1.22V$

$V_o = 400$

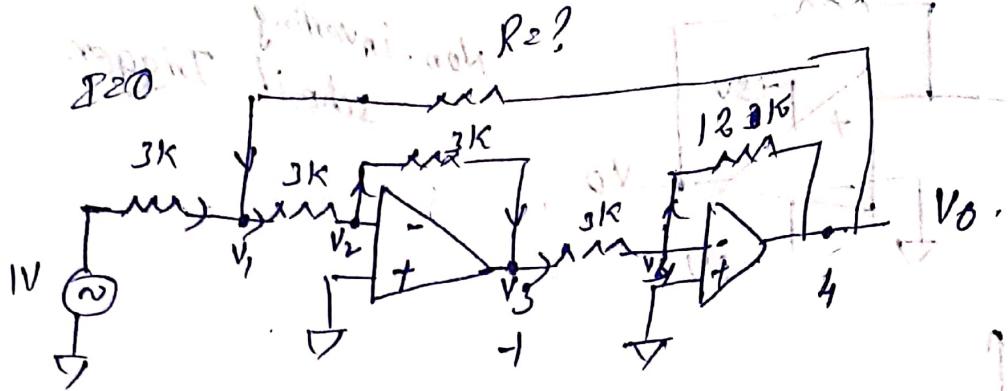

$$\frac{V_1 - 1}{3} = 0$$

$$V_1 = 1 \quad \cancel{\frac{V_1 - V_0}{R}}$$

$$\frac{1 - V_0}{R} + \frac{1 - V_2}{3} = 0$$

$$\frac{V_2 - V_3}{3} + \frac{V_2 - V_0}{12} = 0$$

$$12V_2 = V_3 + V_0$$

$$\frac{V_0 - V_4}{R} + \frac{V_0 - V_0}{R} = 0 \quad V_3 = V_4 + V_3 - V_0 = 0$$

$$V_3 = V_2 + V_4$$

$$2V_2 - 1 = V_2 + V_4$$

$$V_2 = V_3 + 1$$

$$\frac{V_2 - V_3}{3} + \frac{V_4 - V_0}{12} = 0$$

$$5V_4 = 4V_1 + V_0$$

$$5V_4 - 5 = 8V_2 - 4 + V_0$$

$$3(1 - V_0) + R\left(\frac{1 + V_0}{3}\right) + R = 0$$

$$3V_3 + 1 + V_0 = 0$$

$$3V_2 = -1 - V_0$$

$$-V_0 = 3V_2 + 1$$

$$\frac{V_0 - V_4}{1k} + \frac{V_0 - I}{R} = 0$$

$$(V_0 - V_2 - I)R + R(V_0 - I) = 0$$

$$\Rightarrow (12 + R)(V_0 - I) = V_2$$

$$\Rightarrow I = V_0$$

$$\boxed{V_2 = 0}$$

$$\boxed{V_4 = 0}$$

$$\frac{I - V_0}{R} + \frac{I}{3} = 0$$

$$\boxed{3 - 3V_0 + R = 0}$$

$$0V_3 = -1$$


$$\underline{V_0 = 4}$$

$$\frac{V_0 - V_1}{R} + \frac{V_0 - V_4}{R} = 0$$

$$\frac{4 - I}{R} + \frac{4 - 0}{R} = 0$$

$$\frac{3}{R} + \frac{1}{3} = 0$$

$$\underline{R = +9}$$

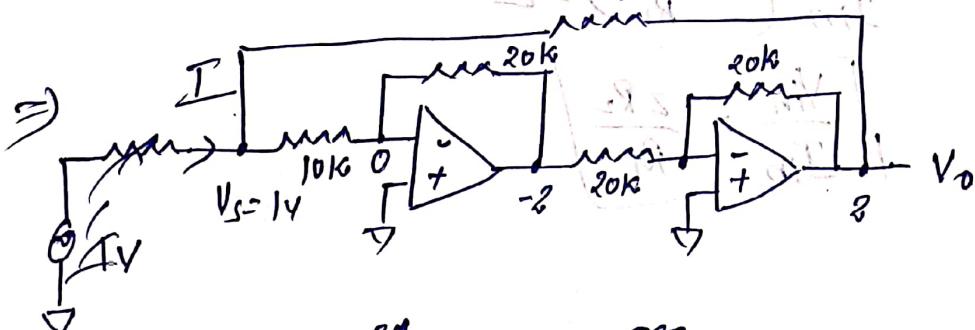


$$-\frac{20}{10}$$

200

$$I = \frac{1 - 0}{10} + \frac{1 - 2}{10 \cdot 1}$$

$$= \frac{1}{10} - \frac{1}{10 \cdot 1}$$
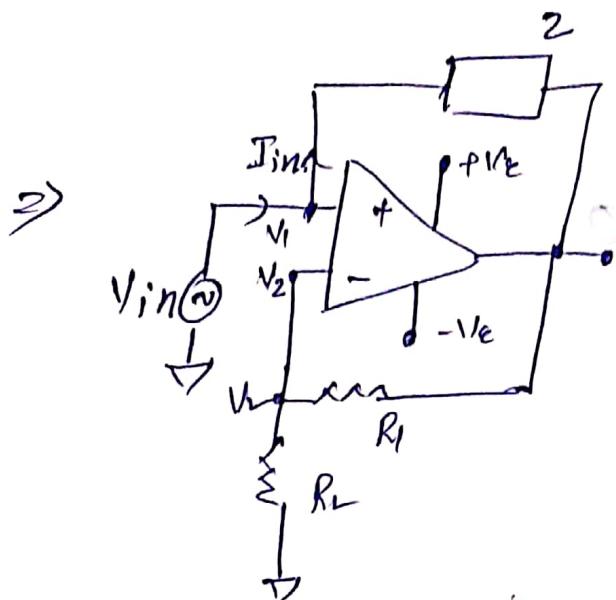
$$\frac{10 \cdot 1 - 10}{10 \cdot 1} = \frac{0 - 1}{10 \cdot 1} = \frac{1}{10 \cdot 10} A = 0.99 mA$$



$$V_0 = \frac{1 + \frac{R_2}{R_1}}{1 - \frac{R_2}{R_1}} V_{in} + \frac{V_2}{R_2} \cdot R_1$$

$$\Delta V = (1 - \frac{R_2}{R_1})(V_0 + V_2)$$

$\Delta V = \Delta V_1$

$$V_0 = V_1$$

$$V_1 = V_{in} - V_2$$

$$\frac{V_2 - V_0}{R_1} + \frac{V_2}{R_2} = 0$$

$$0 = \frac{V_0 - V_2}{R_1} + \frac{V_2 - V_0}{R_2} \quad V_2 \left(\frac{R_1 + R_2}{R_1 R_2} \right) = V_0$$

$$\frac{V_{in} - V_0}{R_1} = I_{in}$$

$$I_{in} = \frac{V_{in}}{R_1} + \frac{V_2}{R_1} \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_2}{R_2}$$

$$\frac{V_{in}}{I_{in}} \left(\frac{R_1}{R_2} \right) = Z$$

$$\boxed{\frac{V_{in}}{I_{in}} = Z R_2}$$

$$= \frac{1}{1 + \frac{R_2}{R_1}} + \frac{1}{1 + \frac{R_2}{R_1}} = 1$$

$$\frac{1}{1 + \frac{R_2}{R_1}} = \frac{1}{Z}$$

$$A_{in} = \frac{1}{Z}$$